

# **MODULE 1**

**Electronic Components, Sources and Measuring Equipment's**

**Premanand S**

Assistant professor


School of Electronics Engineering (SENSE)

Vellore Institute of Technology, Chennai


# OUTLINE

- Evolution of Electronics
- Impact of Electronics in Industry and Society
- Familiarization of Resistors, Capacitors, Inductors | Color Coding – types and specifications
- Electro-mechanical components
- Relay and Contactors
- Regulated Power supply, Function Generator
- Multimeter
- CRO

# TECHNOLOGY VS ELECTRONICS

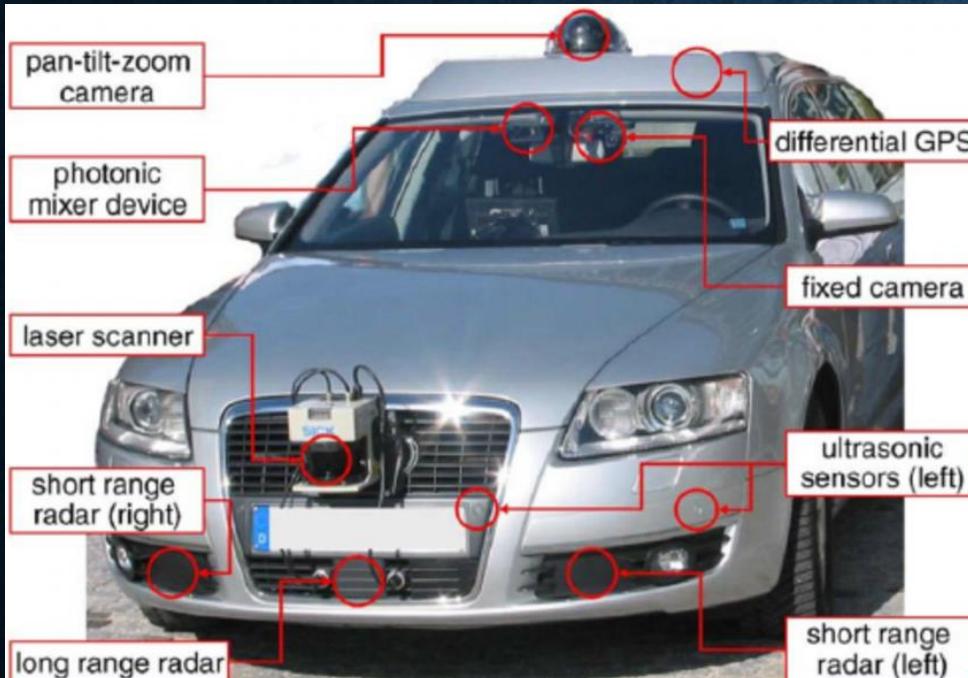



# TECHNOLOGY VS ELECTRONICS

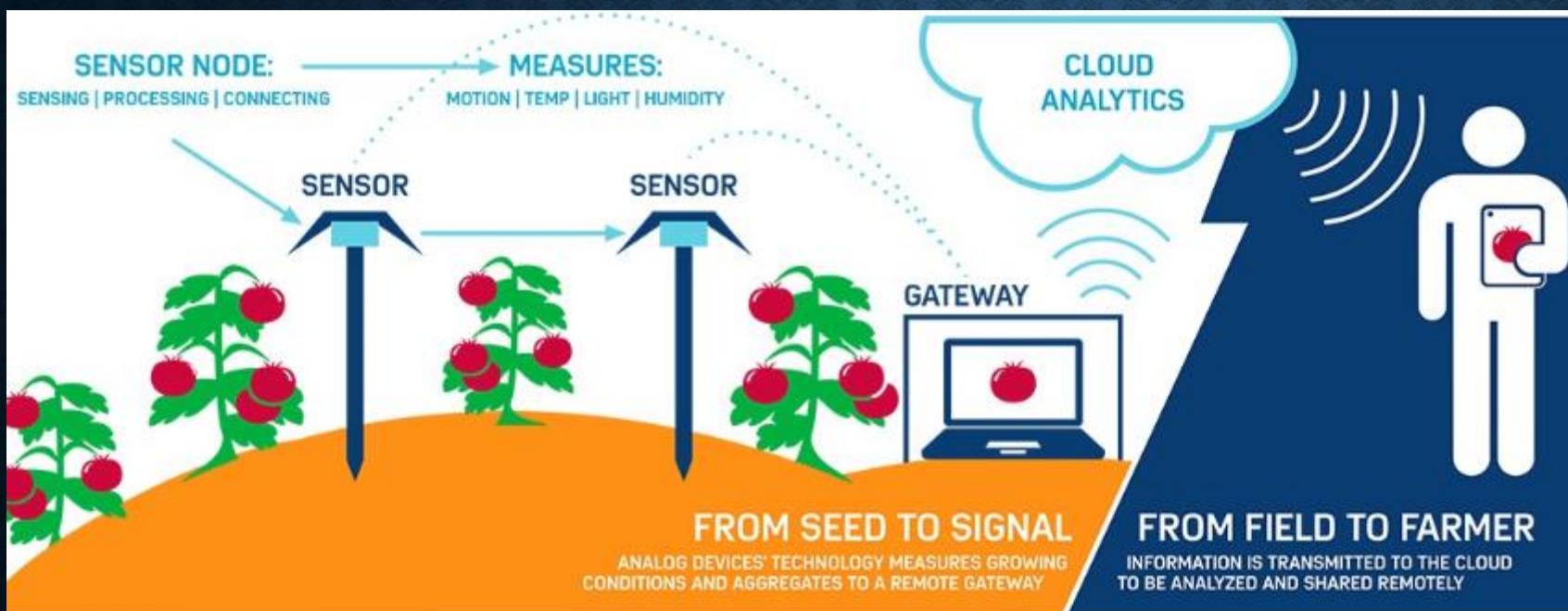


# TECHNOLOGY VS ELECTRONICS



# TECHNOLOGY VS ELECTRONICS

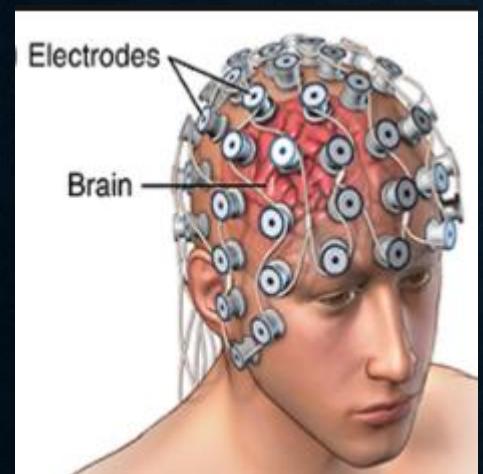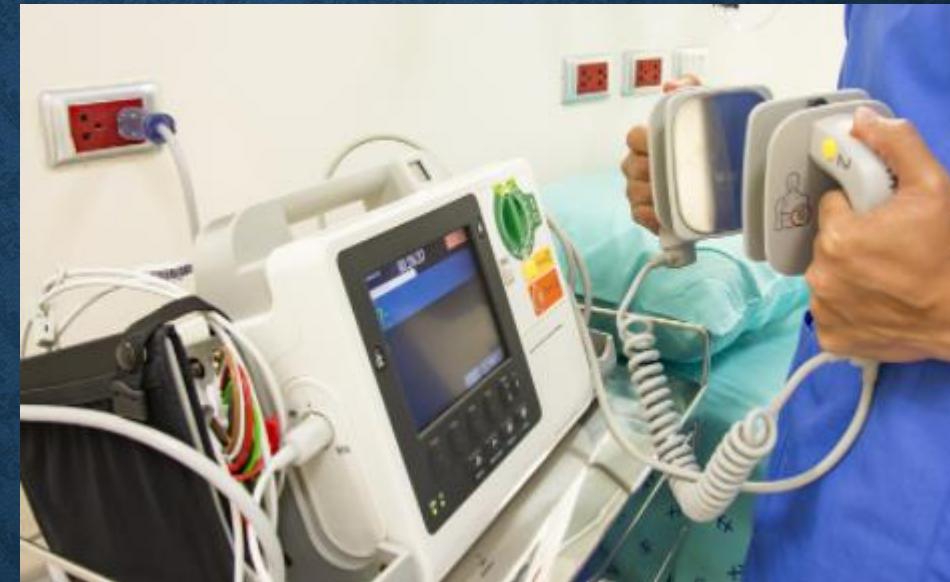


# TECHNOLOGY VS ELECTRONICS

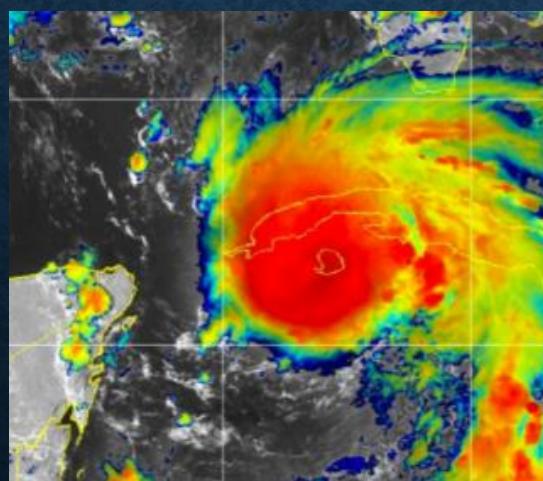

# HISTORY OF ELECTRONICS


- There will be many inventions, but some breakthrough inventions for electronics are,
  - Vacuum tubes (Gas)
  - Transistors (Semiconductors)
  - Integrated circuits (IC/chip)
  - Microprocessor
  - Artificial Intelligence

# EVOLUTION OF ELECTRONICS

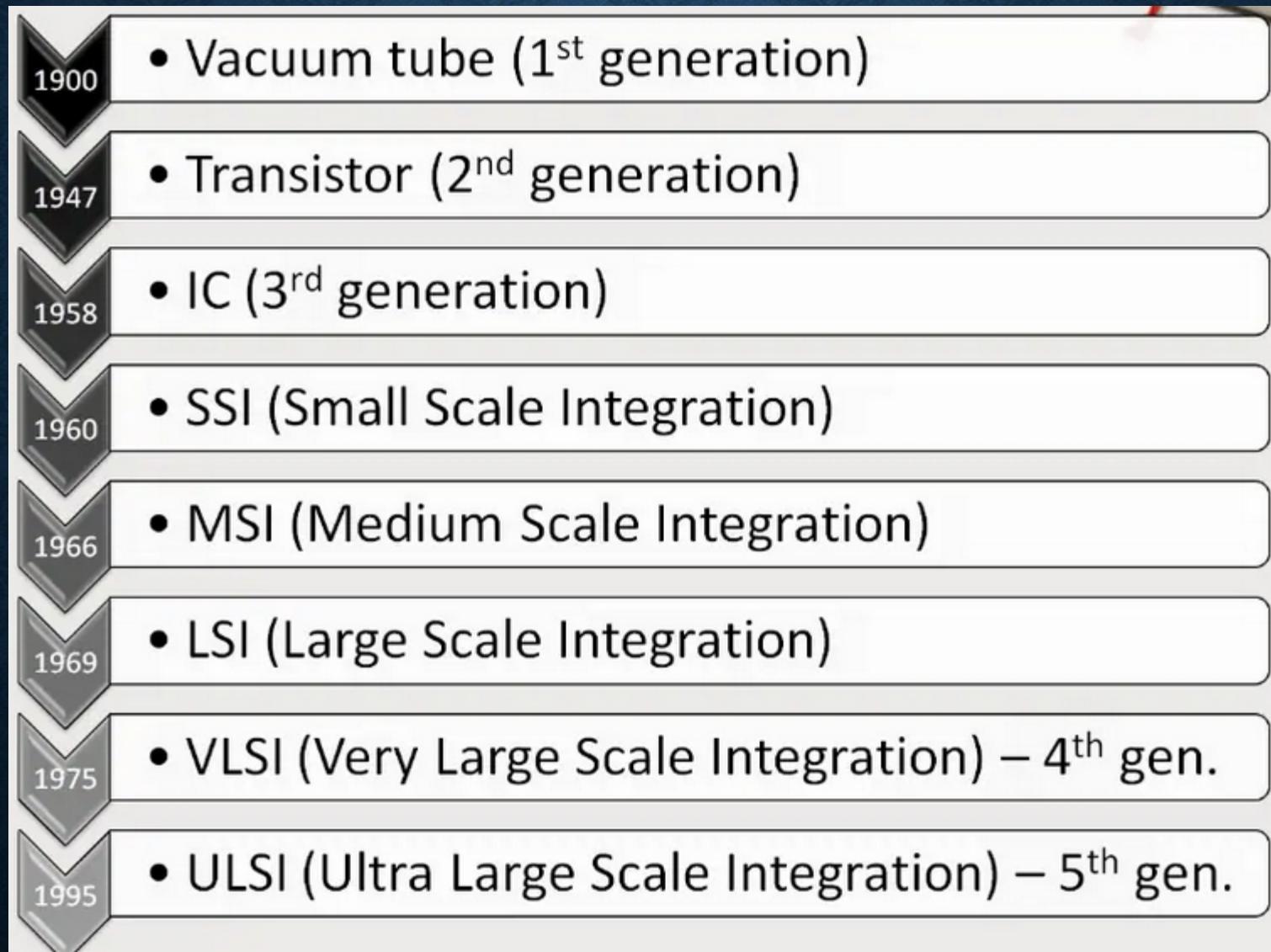
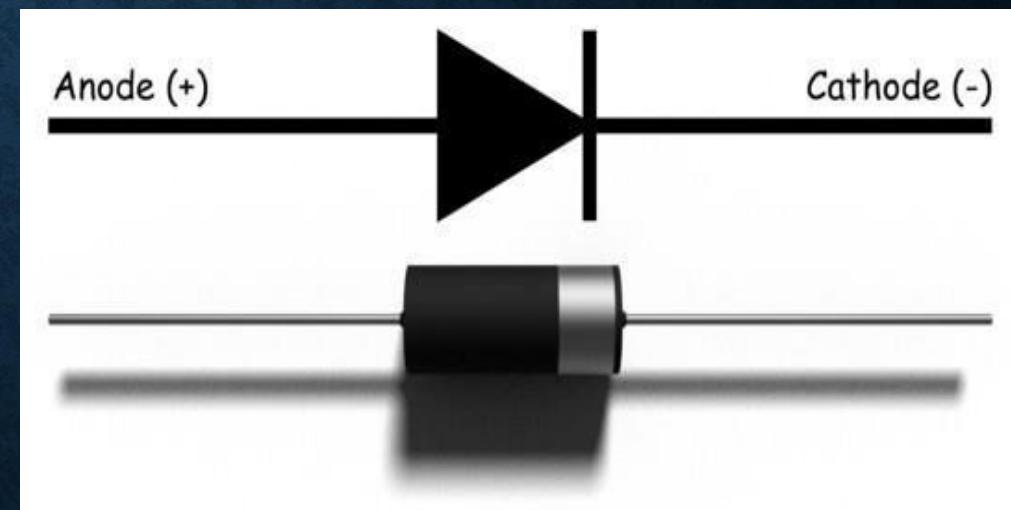
# VACUUM TUBE

- The simplest vacuum tube, the diode
- Invented in 1904 by John Ambrose Fleming,
- Contains only a heated electron-emitting cathode and an anode.
- Electrons can only flow in one direction through the device (from the cathode to the anode)





# HOW VACUUM TUBE WORKS?

- <https://www.youtube.com/watch?v=A7M1zcLfBKg&t=2s>

# TRANSISTOR


- A transistor can act as a switch or gate for electronic signals, opening and closing an electronic gate many times per second.
- It ensures the circuit is ON if the current is flowing and switched off if it isn't
- Semiconductor device | used to amplify or switch electronic signals and electrical power, Usually with at least three terminals for connection to an external circuit.

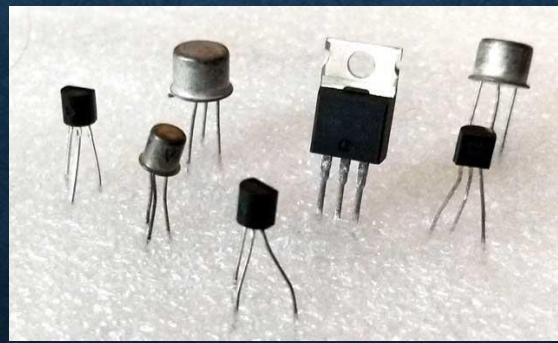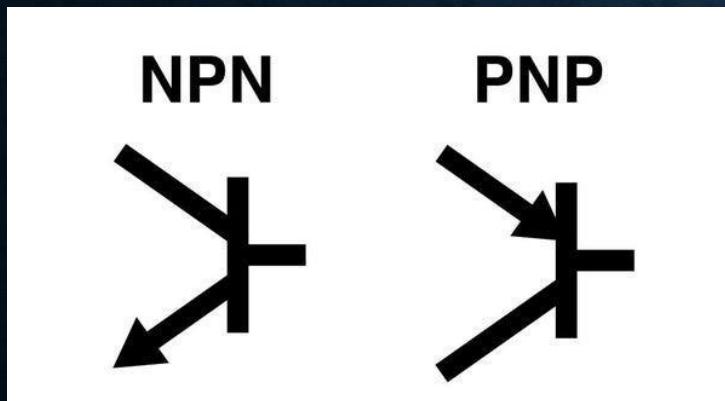

1. Emitter
2. Base
3. Collector

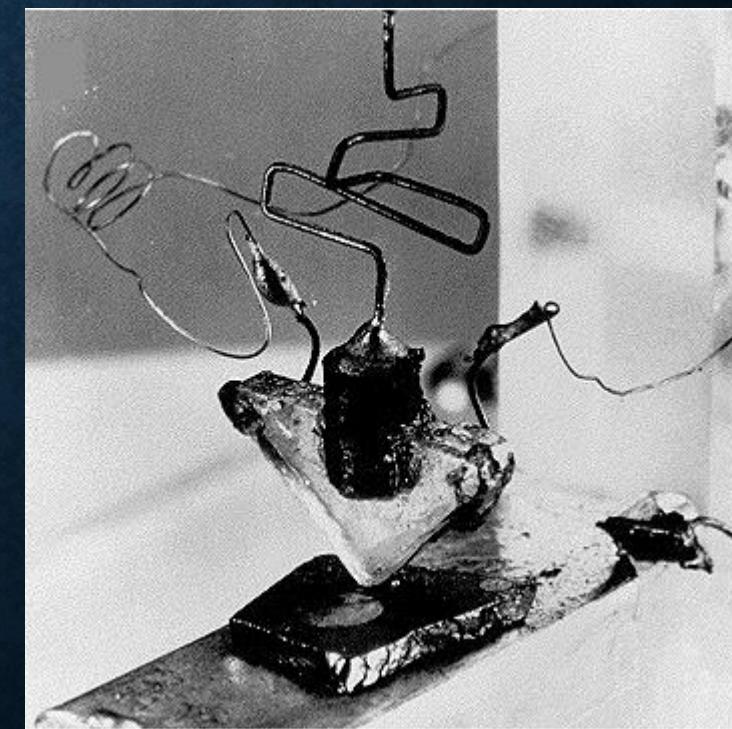
# POINT TRANSISTORS

- 1947, John Bardeen, Walter Brattain and William Shockely, Bell Lab
- Revolutionized electronic industry
- Made it possible to develop an electronic computer
- Smaller and more efficient than its predecessors
- Field of electronics shifted from vacuum tubes (bulky and fragile device which consumed a significant power) to solid state devices
- Light weight, reliability, low cost and less power



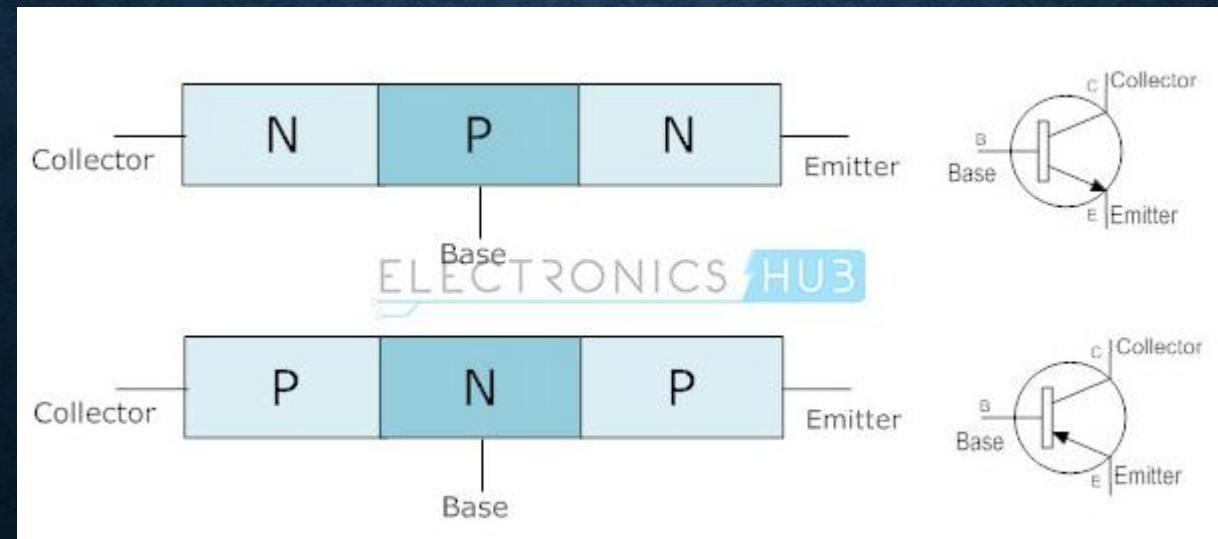
# JUNCTION TRANSISTORS

- William Shockley, Bell Lab
- A transistor consists of three layers of semi conductor material
- Each layer is having the capability of transferring current to the other layers.
- Relatively bulky devices that were difficult to manufacture on a mass production basis


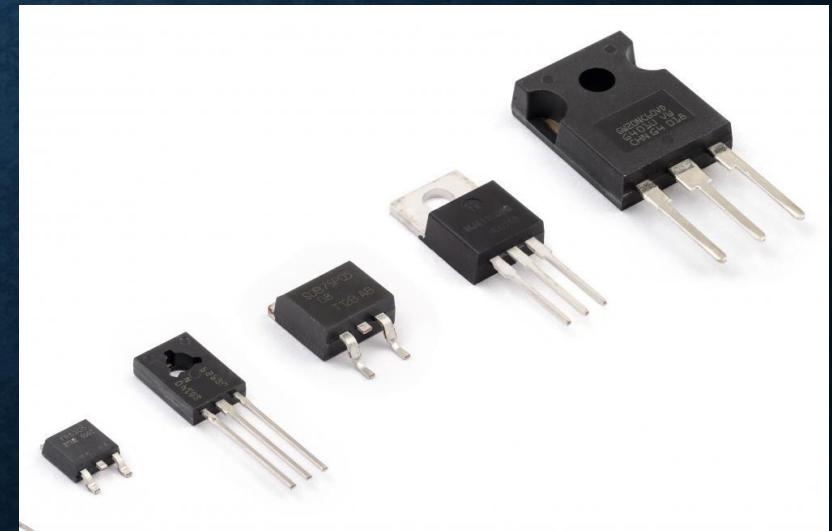
# SILICON TRANSISTORS

- First commercial transistor was used in telephonic equipment
- Military computers in 1952
- In 1953 transistor is used in medical device (Hearing aid)
- First transistor is made of semiconductor material, polycrystals of Germanium (Ge) in 1950s





# SILICON TRANSISTORS

- Silicon (Si) replaced Ge with the development of techniques for purifications and crystal growth
- Si was considered as a better material due to less temperature sensitive resulting from relatively larger band gap
- Due to successful performance at high temperatures silicon transistor are used from the year 1954
- Beginning of sixties techniques were developed for integration of transistors, resistors and capacitors on a silicon chip


# FIELD EFFECT TRANSISTOR

- 1959 Field effect transistor (MOSFET), Invented by Mohamed M. Atalla and Dawon Kahng at Bell Labs in 1959
- Consists of three layers metal (M-gate) ,Oxide(O-insulation ), silicon (S-semiconductor)
- Basic element in most modern electronic equipment
- Most widely used electronic device in the world
- First truly compact transistor miniaturized and mass-produced

## TYPES OF FIELD EFFECT TRANSISTORS

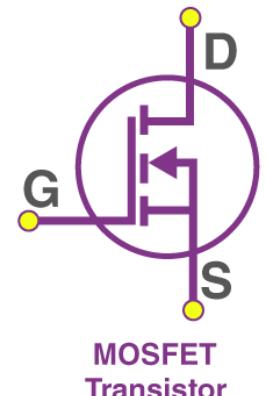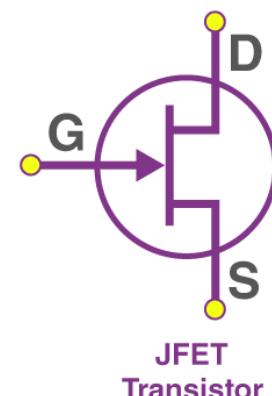


# TRANSISTOR - ADVANCEMENT

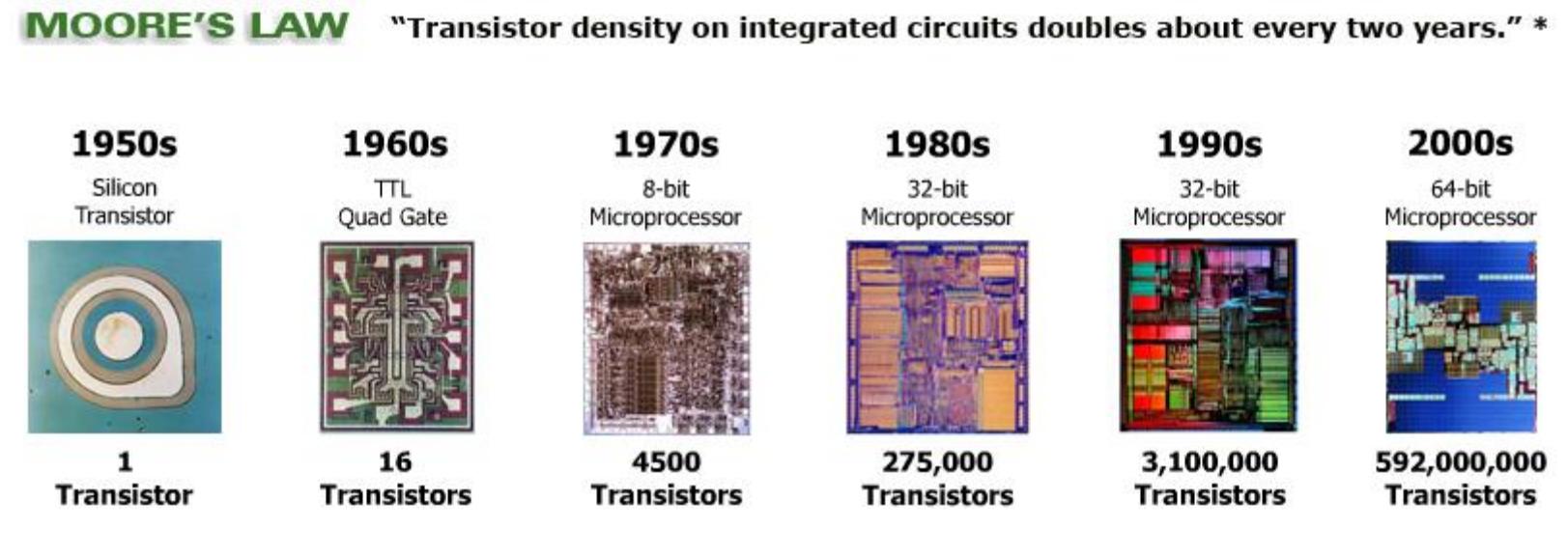


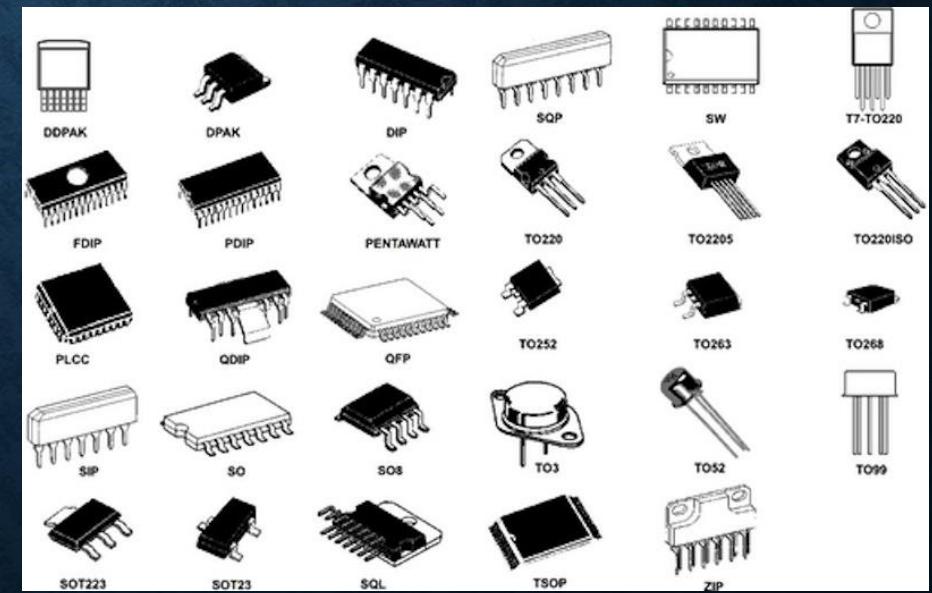
# INTEGRATED CIRCUIT (IC)

- Integration of larger number of electronic components on a single chip
- Beginning of microelectronics revolution
- 1958 Jack Kilby Texas instrument demonstrated first integrated circuit (IC/chip)


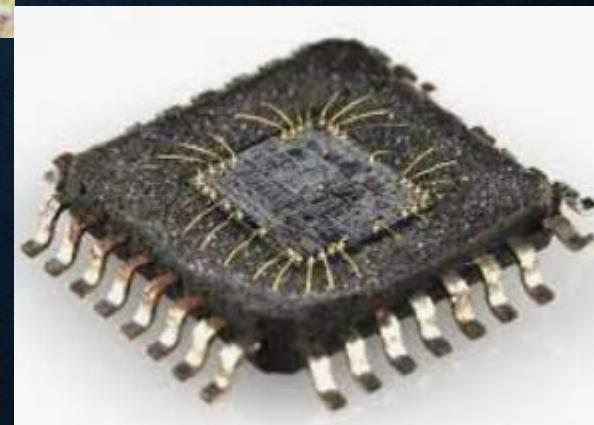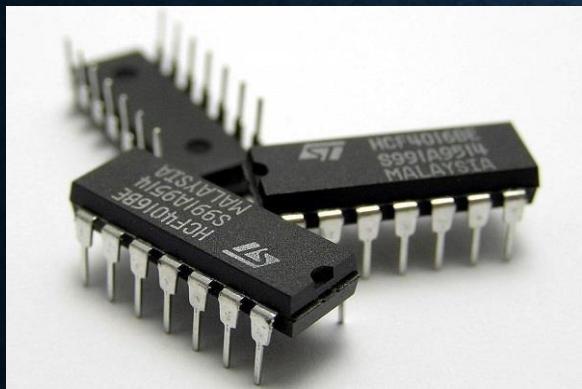
# INTEGRATED CIRCUIT (IC)

- Chip or microchip, is a semiconductor wafer on which a thousand or millions of tiny resistors, capacitors, and transistors are fabricated.




# MICROPROCESSOR

- Thousands of integrated circuits were built onto a single silicon chip.
- Uses LOGIC (processes data)
- Can move data from one memory location to another.
- Can make decisions



# SEMICONDUCTOR'S REACH

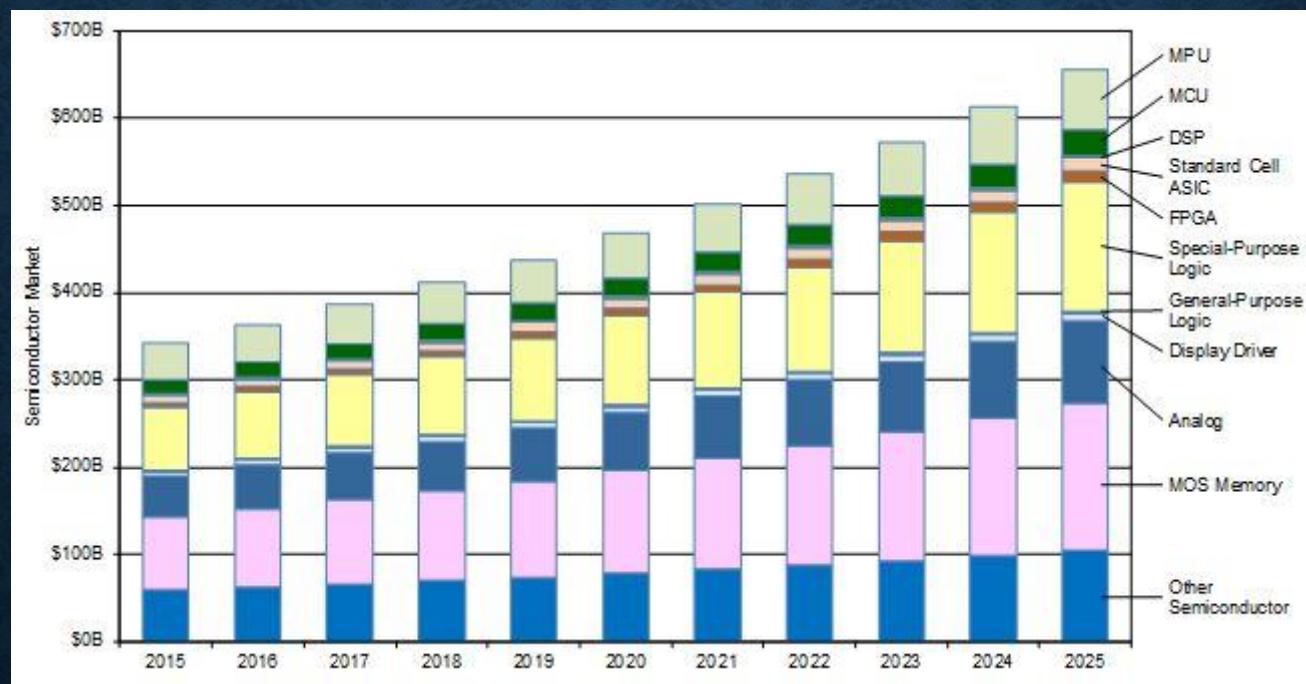

# **ARTIFICIAL INTELLIGENCE**

- Biometric Detection and Recognition
- Human computer Interaction
- Email Spam and Malware Filtering
- Search Engine
- Social Media Services
- Surveillance and tracking
- Virtual Personal Assistants
- Online Customer Support
- Online shopping
- Cyber Security
- .....

# **IMPACT OF ELECTRONICS**

- Communication
  - Telegram, Telephone, Fax, Radio, Mobile communication, Teleconference
- Military
  - RADAR, SONAR, Missile/Rocket launching, Wearable electronics
- Entertainment
  - TV, Social media, video game etc

# **IMPACT OF ELECTRONICS – CONT....**

- Education
  - Online classes
- Automobile
  - ACB, GPS, driverless car
- Medical
  - ECG, EEG, X-Ray, MRI, CT scan, Telemedicine, Bio sensors etc

# BASIC TERMINOLOGIES



- **Charge (Q)** – most basic quantity in electric circuit.
- **Current (I)** – rate of change of charge passing through a conductor.
  - **direct current (DC)** – constant current
  - **alternating current (ac)** – time-varying current
- **Voltage (V)** – energy required to move a charge.
  - **DC voltage** – constant voltage
  - **ac voltage** – sinusoidal time-varying voltage
- **Power (P)** – rate of expending energy
  - **instantaneous power** – time-varying power ( $p = vi$ )
- **Energy (E)** – capacity to do work.

# **TYPES OF COMPONENTS**


- Active Electronics
- Passive Electronics
- Electromechanical

## ACTIVE

## PASSIVE

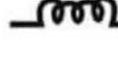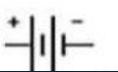Transistor			Resistor		
Diode			LDR		
LED			Thermistor		
Photodiode			Capacitor		
Integrated Circuit		-	Inductor		
Operational Amplifier			Switch		
Seven Segment Display			Variable Resistor		
Battery			Transformer		

# ELECTROMECHANICAL COMPONENTS

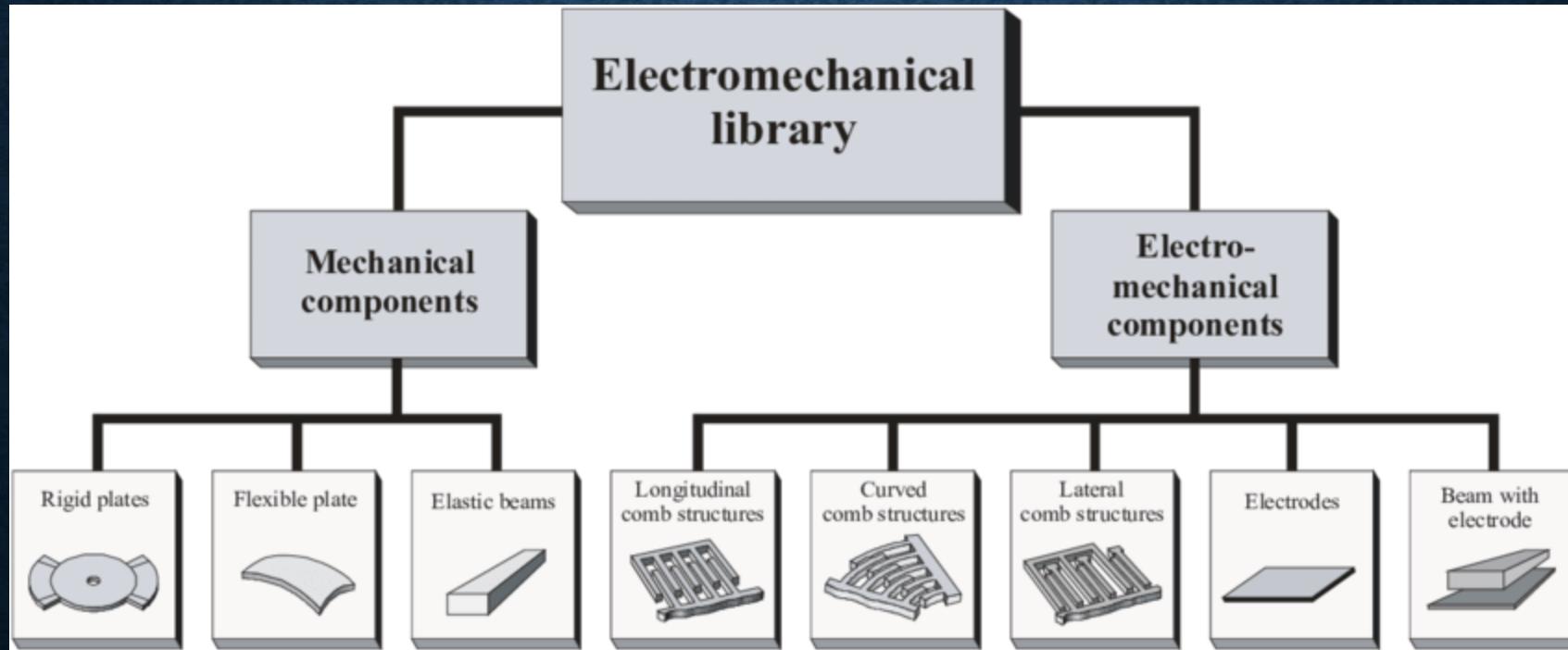

# **ELECTRONIC COMPONENTS**



Battery



Resistor

# Stores energy




Inductor




Capacitor

# RESISTOR

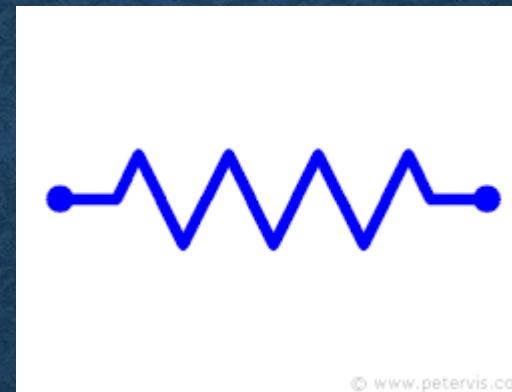


© www.petervis.com

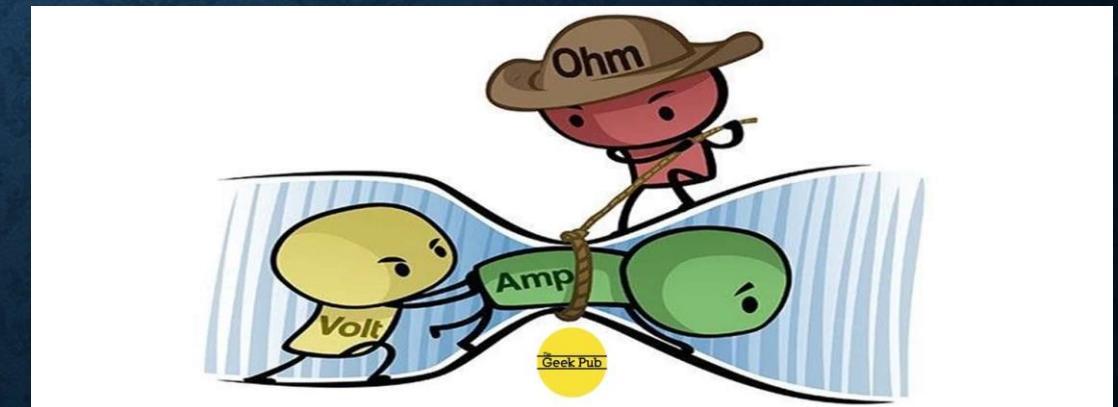

# RESISTOR

- Electronic component that opposes the flow of current in an electrical circuit
- Resists – oppose the flow of current | control the current | Safety
- Resistance - ratio of voltage applied across a resistor terminal to the intensity of current through circuit |  $V = IR$  or  $R = V/I$
- Maintain stable resistance value, even when temperature of the environment changes
- Why important? Useful energy transfer as they are used to control the flow of current.  
Ex: Element in the kettle turns electric energy to heat energy – boil water
- Types : Fixed and variable resistor (Dimmer light & Volume control knobs on radios)

# RESISTOR CODING

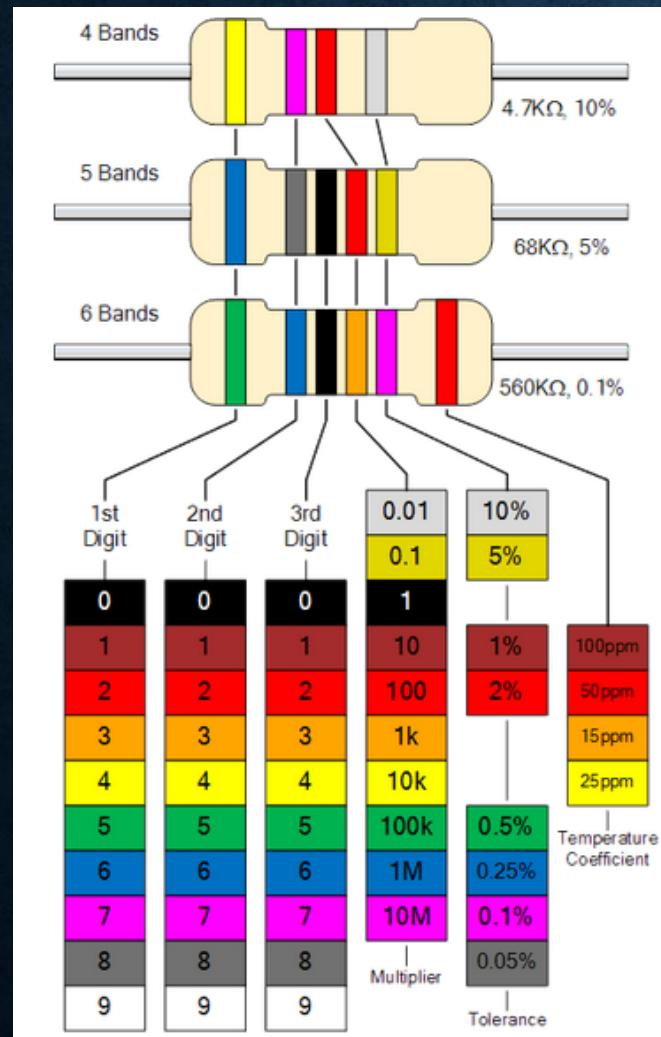

Digit, Digit, Multiplier = Colour, Colour  $\times 10^{\text{colour}}$  in Ohm's (Ω)

Yellow Violet Red = 4 7 2 = 4 7  $\times 10^2$  = 4700Ω  
or 4k7 Ohm

Colour	Digit	Multiplier	Tolerance
Black	0	1	
Brown	1	10	± 1%
Red	2	100	± 2%
Orange	3	1,000	
Yellow	4	10,000	
Green	5	100,000	± 0.5%
Blue	6	1,000,000	± 0.25%
Violet	7	10,000,000	± 0.1%
Grey	8		± 0.05%
White	9		
Gold		0.1	± 5%
Silver		0.01	± 10%
None			± 20%

# 3, 4, 5 & 6 BAND RESISTOR

Number of Coloured Bands	3 Coloured Bands (E6 Series)	4 Coloured Bands (E12 Series)	5 Coloured Bands (E48 Series)	6 Coloured Bands (E96 Series)
1 <sup>st</sup> Band	1 <sup>st</sup> Digit	1 <sup>st</sup> Digit	1 <sup>st</sup> Digit	1 <sup>st</sup> Digit
2 <sup>nd</sup> Band	2 <sup>nd</sup> Digit	2 <sup>nd</sup> Digit	2 <sup>nd</sup> Digit	2 <sup>nd</sup> Digit
3 <sup>rd</sup> Band	Multiplier	Multiplier	3 <sup>rd</sup> Digit	3 <sup>rd</sup> Digit
4 <sup>th</sup> Band	–	Tolerance	Multiplier	Multiplier
5 <sup>th</sup> Band	–	–	Tolerance	Tolerance
6 <sup>th</sup> Band	–	–	–	Temperature Coefficient

# RESISTOR COLOUR CODING

- <https://www.calculator.net/resistor-calculator.html?bandnum=4&band1=brown&band2=green&band3=blue&multiplier=violet&tolerance=gold&temperatureCoefficient=brown&type=c&x=119&y=19>
- In order to know the use the range <https://www.allaboutcircuits.com/tools/resistor-color-code-calculator/>

# **TYPES OF RESISTOR**

- **FIXED RESISTOR**

- Carbon Composite

- Film

- Wire Wound

- Resistance Wire

- **VARIABLE RESISTOR**

- Rheostat

- Potentiometer

- Thermistor

- Humistor

- Varistor

- Photoresistor

# CONNECTION - RESISTOR


- Series

Current remains CONSTANT

$$I = I_1 = I_2 = I_3 = \dots = I_n$$

Voltage ADDS up

$$V = V_1 + V_2 + V_3 + \dots + V_n$$

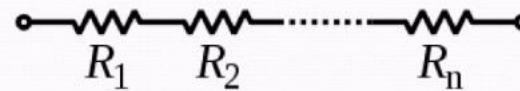

$$R_{\text{eq}} = R_1 + R_2 + \dots + R_n$$

- Parallel


Current ADDS up

$$I = I_1 + I_2 + I_3 + \dots + I_n$$

Voltage remains CONSTANT

$$V = V_1 = V_2 = V_3 = \dots = V_n$$

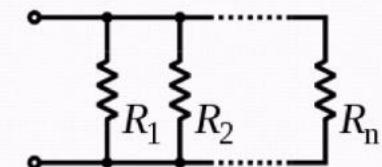
$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$



# POWER RATING - RESISTOR


- Ohms Law :  $V = I \times R$
- Power rating:  $P = V \times I = I \times R \times I = I^2 R = V^2 / R$
- Note: Larger the POWER, Greater the Physical size of the Resistor

# RESISTOR - SERIES

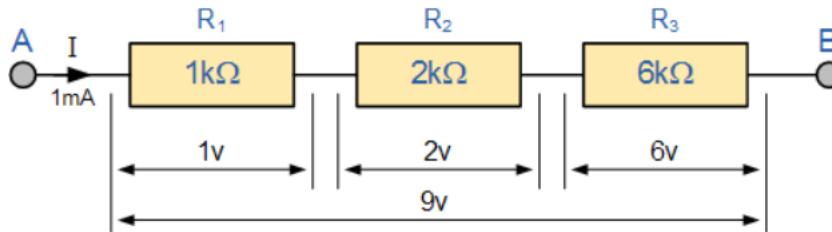

$$R_T = R_1 + R_2 + R_3$$

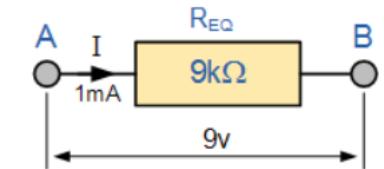
$$I_{R1} = I_{R2} = I_{R3} = I_{AB} = 1\text{mA}$$




$$R_{EQ} = R_1 + R_2 + R_3 = 1\text{k}\Omega + 2\text{k}\Omega + 6\text{k}\Omega = 9\text{k}\Omega$$

a single value of resistance that can replace any number of resistors in series without altering the values of the current or the voltage in the circuit

# RESISTOR - SERIES

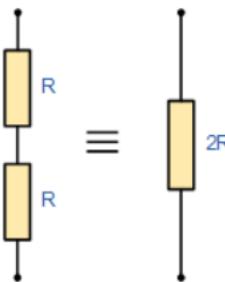

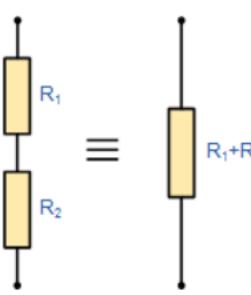If two resistances or impedances in series are equal and of the same value, then the total or equivalent resistance,  $R_T$  is equal to twice the value of one resistor. That is equal to  $2R$  and for three equal resistors in series,  $3R$ , etc.



If two resistors or impedances in series are unequal and of different values, then the total or equivalent resistance,  $R_T$  is equal to the mathematical sum of the two resistances. That is equal to  $R_1 + R_2$ . If three or more unequal (or equal) resistors are connected in series then the equivalent resistance is:  $R_1 + R_2 + R_3 + \dots$ , etc.

# RESISTOR - SERIES

$$V_{AB} = V_{R1} + V_{R2} + V_{R3} = 9V.$$

Using Ohm's Law, the voltage across the individual resistors can be calculated as:

$$\text{Voltage across } R_1 = IR_1 = 1\text{mA} \times 1\text{k}\Omega = 1\text{V}$$


$$\text{Voltage across } R_2 = IR_2 = 1\text{mA} \times 2\text{k}\Omega = 2\text{V}$$

$$\text{Voltage across } R_3 = IR_3 = 1\text{mA} \times 6\text{k}\Omega = 6\text{V}$$

$$V_{\text{Total}} = V_{R1} + V_{R2} + V_{R3} + \dots + V_N$$
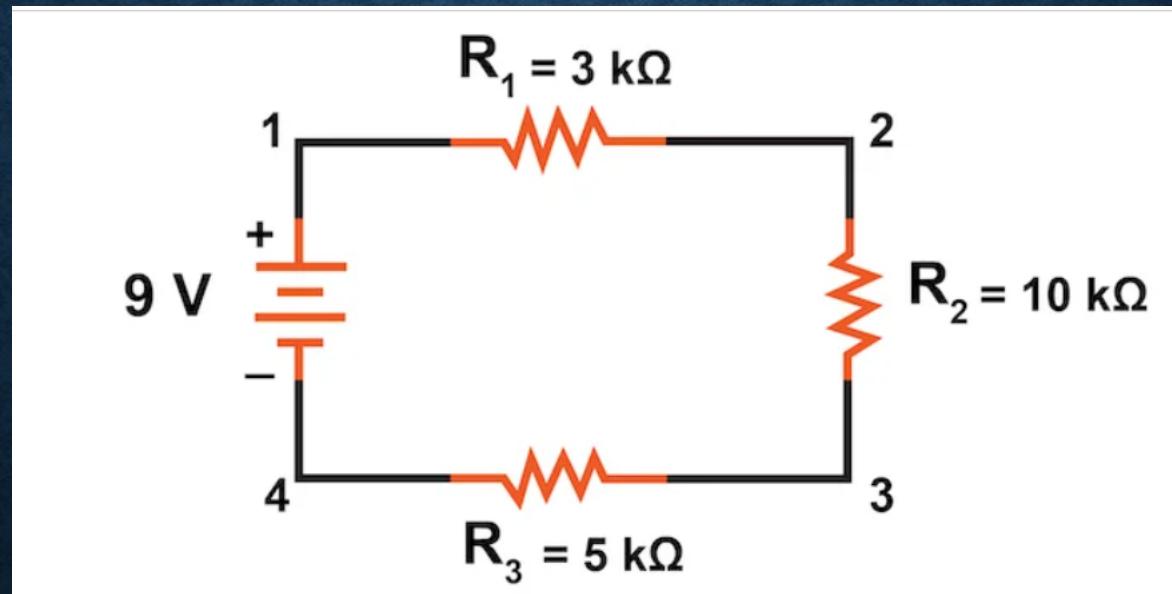
# RESISTOR – SERIES #01


- Current:** The current is the same through each component in a series circuit
- Resistance:** The total resistance of a series circuit is equal to the sum of the individual resistances.
- Voltage:** The total voltage drop in a series circuit equals the sum of the individual voltage drops.



# CURRENT IN A SERIES CIRCUIT

- **Current:** The current is the same through each component in a series circuit
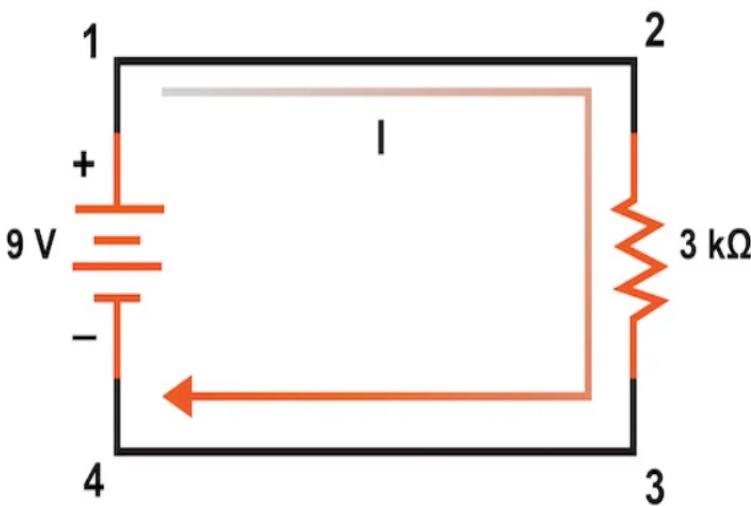
# USING OHM'S LAW IN A SINGLE RESISTOR CIRCUIT




- Since the circuit has 9 V of electromotive force between points 1 and 4 (directly across the battery), it must also drop 9 V between points 2 and 3 (directly across the resistor)
- Because Kirchhoff's Voltage law states that the sum of all voltages in a loop must equal zero

$$I = \frac{V}{R}$$

$$I = \frac{9 \text{ V}}{3 \text{ k}\Omega} = 3 \text{ mA}$$
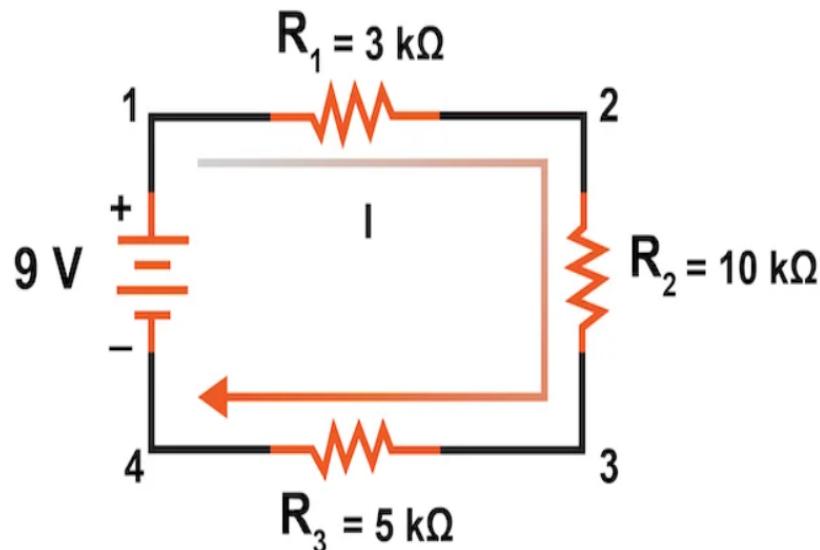
# USING OHM'S LAW FOR SERIES CIRCUITS WITH MULTIPLE RESISTORS



- 9 V between points 1 and 4, which is the amount of electromotive force driving the current through the series combination of  $R_1$ ,  $R_2$ , and  $R_3$ .
- However, we cannot take the value of 9 V and divide it by  $3 \text{ k}\Omega$ ,  $10 \text{ k}\Omega$ , or  $5 \text{ k}\Omega$  to try to find a current value because we don't know how much voltage is across any one of those resistors individually.
- The voltage value of 9 V is the total quantity for the whole circuit, whereas the values of  $3 \text{ k}\Omega$ ,  $10 \text{ k}\Omega$ , or  $5 \text{ k}\Omega$  are individual quantities for individual resistors.

$$I_{R1} = \frac{V_{R1}}{3 \text{ k}\Omega}$$


$$E_{R1} = I_{R1} \cdot 3 \text{ k}\Omega$$

# USING OHM'S LAW TO CALCULATE CIRCUIT CURRENT IN A SERIES CIRCUIT

$$I_{total} = \frac{V_{total}}{R_{total}}$$

$$I_{total} = \frac{9 \text{ V}}{18 \text{ k}\Omega} = 500 \mu\text{A}$$
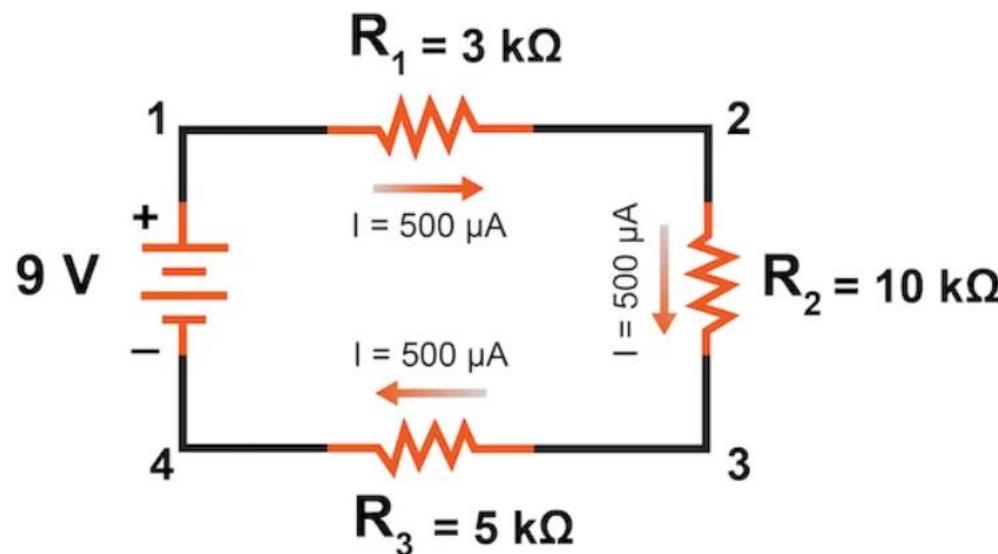
# HOW TO CALCULATE VOLTAGE DROP IN A SERIES CIRCUIT



$$V_{R1} = I_{R1} \cdot R_1 = (500 \mu\text{A}) \cdot (3 \text{ k}\Omega) = 1.5 \text{ V}$$

$$V_{R2} = I_{R2} \cdot R_2 = (500 \mu\text{A}) \cdot (10 \text{ k}\Omega) = 5.0 \text{ V}$$

$$V_{R3} = I_{R3} \cdot R_3 = (500 \mu\text{A}) \cdot (5 \text{ k}\Omega) = 2.5 \text{ V}$$

Notice that sum of the voltage drops ( $1.5 + 5.0 + 2.5 = 9.0 \text{ V}$ ) is equal to the battery (supply) voltage of 9 V


# HOW TO CALCULATE TOTAL RESISTANCE IN A SERIES CIRCUIT

- The total resistance of a series circuit is equal to the sum of the individual resistances.

$$R_{total} = R_1 + R_2 + R_3$$

$$R_{total} = 3 \text{ k}\Omega + 10 \text{ k}\Omega + 5 \text{ k}\Omega$$


$$R_{total} = 18 \text{ k}\Omega$$

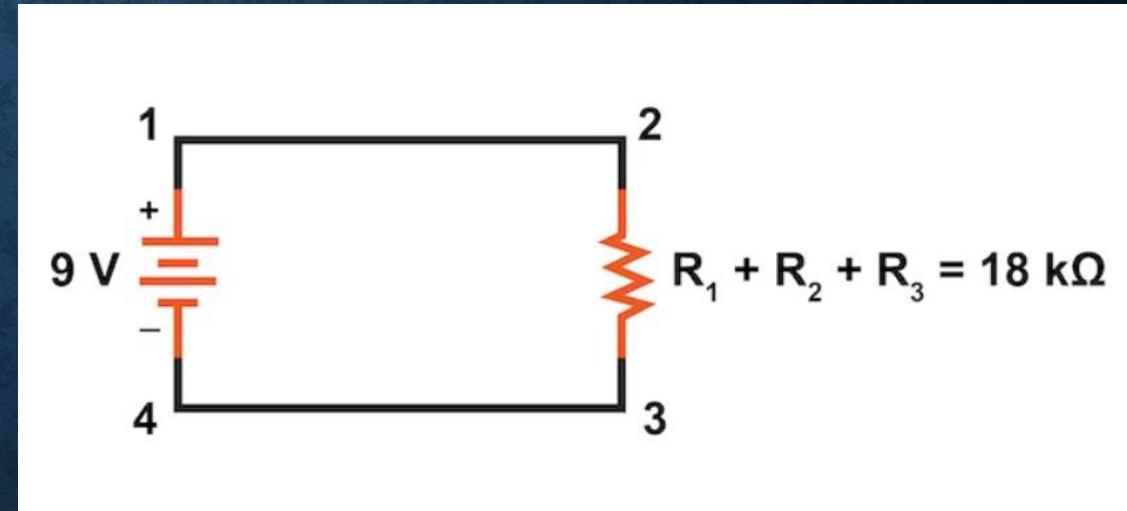

# SERIES CIRCUIT FUNDAMENTALS

- All components in a series circuit conduct the same current:  $I_{\text{total}} = I_1 = I_2 = \dots I_n$
- The total equivalent resistance of a series circuit is equal to the sum of the individual resistances:  $R_{\text{total}} = R_1 + R_2 + \dots R_n$
- The total voltage drop in a series circuit is equal to the sum of the individual voltage drops  $V_{\text{total}} = V_1 + V_2 + \dots V_n$


# RESISTOR – SERIES #02

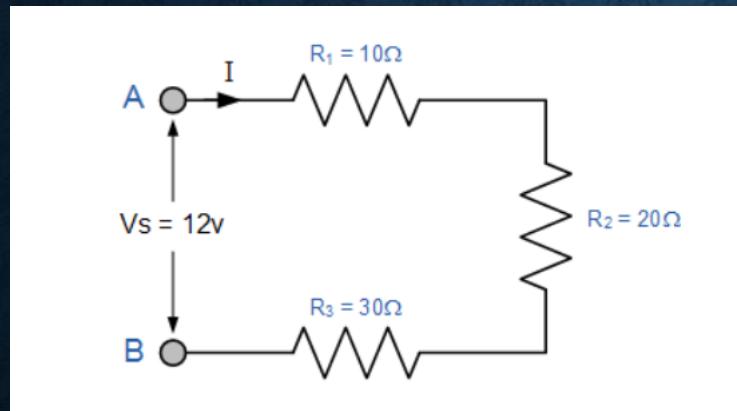

Resistance	Current	Voltage	Power
$R_1 = 10\Omega$	$I_1 = 200mA$	$V_1 = 2V$	$P_1 = 0.4W$
$R_2 = 20\Omega$	$I_2 = 200mA$	$V_2 = 4V$	$P_2 = 0.8W$
$R_3 = 30\Omega$	$I_3 = 200mA$	$V_3 = 6V$	$P_3 = 1.2W$
$R_T = 60\Omega$	$I_T = 200mA$	$V_S = 12V$	$P_T = 2.4W$
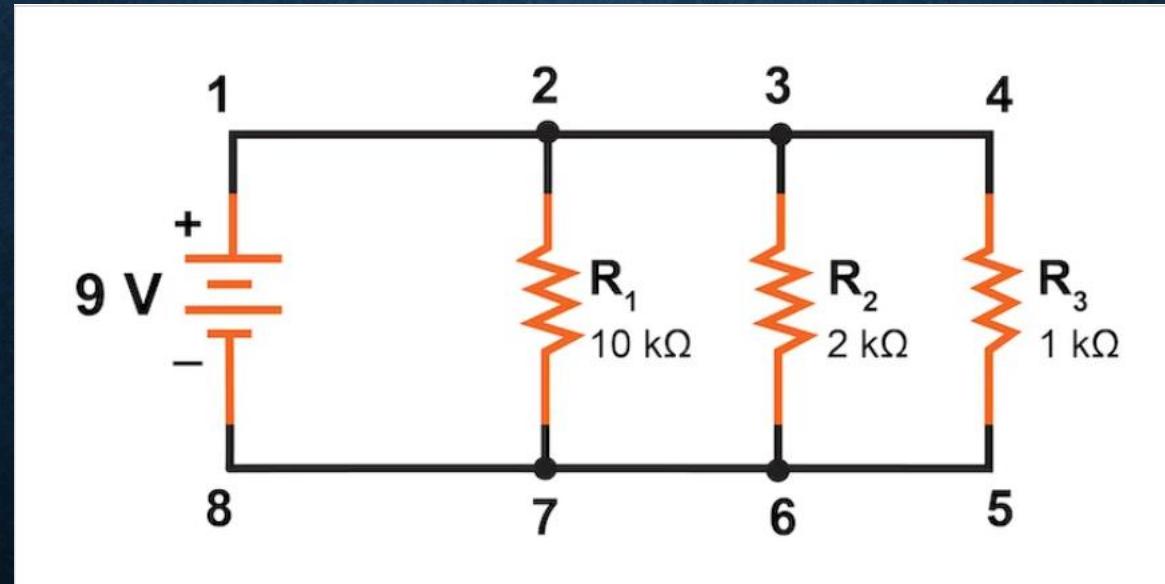
# RESISTOR - PARALLEL

- **Voltage:** The voltage is equal across all components in a parallel circuit.
- **Current:** The total circuit current equals the sum of the individual branch currents.
- **Resistance:** The total resistance of a parallel circuit is *less than* any of the individual branch resistances.



# RESISTOR - PARALLEL

- First principle - Parallel circuits is that the voltage is equal across each parallel component
- There are only two sets of electrically common points in a parallel circuit, and the voltage measured between sets of common points must always be the same at any given time.
- Nodes 1, 2, 3, and 4 are the same electrical node.
- Likewise, nodes 5, 6, 7, and 8 are the same electrical node
- Voltage across  $R_1$  is equal to the voltage across  $R_2$ , which is equal to the voltage across  $R_3$ , and is then equal to the voltage across the battery (9 V).


# USING OHM'S LAW FOR PARALLEL CIRCUITS TO DETERMINE CURRENT

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{9 \text{ V}}{10 \text{ k}\Omega} = 0.9 \text{ mA}$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{9 \text{ V}}{2 \text{ k}\Omega} = 4.5 \text{ mA}$$

$$I_{R3} = \frac{V_{R3}}{R_3} = \frac{9 \text{ V}}{1 \text{ k}\Omega} = 9.0 \text{ mA}$$

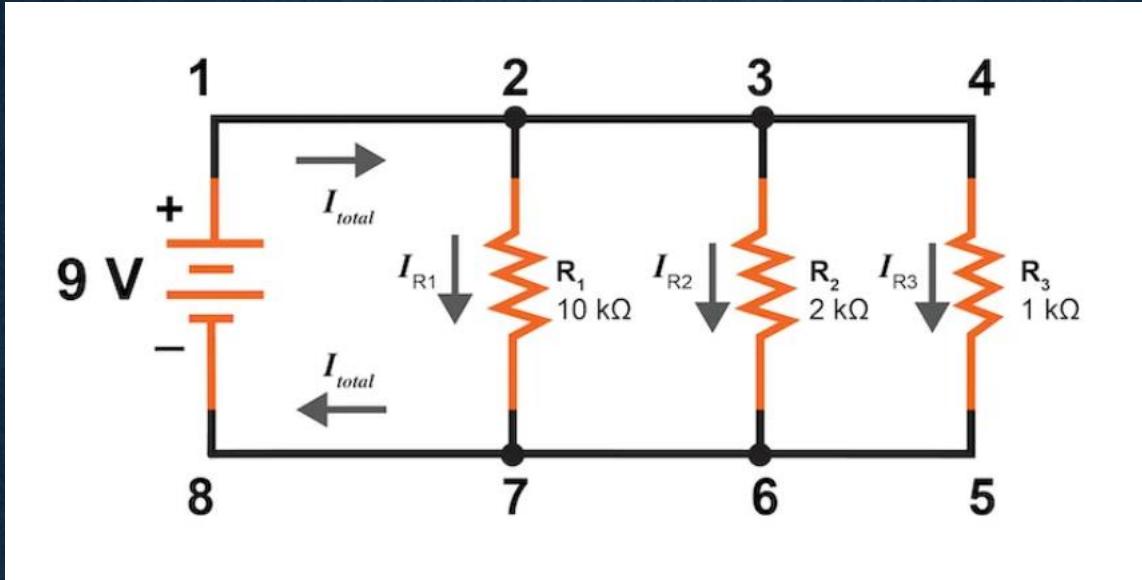we still don't know the total current or total resistance for this parallel circuit. Despite that, if we think carefully about what is happening, it should become apparent that the total current must equal the sum of all individual resistor ("branch") currents



river branching into several smaller streams, the combined flow rates of all streams must equal the flow rate of the whole river

$$I_{total} = I_{R1} + I_{R2} + I_{R3} = 0.9 + 4.5 + 9.0 = 14.4 \text{ mA}$$

This is the second principle of parallel circuits: the total parallel circuit current equals the sum of the individual branch currents.

# HOW TO CALCULATE TOTAL RESISTANCE IN A PARALLEL CIRCUIT

$$R_{total} = \frac{V_{total}}{I_{total}} = \frac{9 \text{ V}}{14.4 \text{ mA}} = 625\Omega$$

The total circuit resistance is only  $625 \Omega$ . This is *less* than any one of the individual resistors.

In a series circuit, the total resistance is the sum of the individual resistances and is, therefore, always *greater* than any of the resistors individually.

However, here in the parallel circuit, the opposite is true. Each parallel resistor added to a circuit reduces the total equivalent resistance. Mathematically, the relationship between total resistance and individual resistance in a parallel circuit looks like this

$$R_{total} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


- If we think of our parallel circuit in terms of conductance rather than resistance, this often makes more sense. The conductance of a parallel circuit is the sum of the individual branch conductance's as the circuit gets more conductive as we add more paths for currents to flow

$$G_{total} = G_1 + G_2 + G_3$$

# RESISTOR - PARALLEL


- The voltage is the same for all components in a parallel circuit:  $V_1 = V_2 = \dots V_n$
- The total parallel circuit current is the sum of the individual branch currents:  $I_{\text{total}} = I_1 + I_2 + \dots I_n$
- The total resistance of a parallel circuit is **less** than any of the individual brand resistances:  $R_{\text{total}} = 1/(1/R_1 + 1/R_2 + 1/R_3)$

# PARALLEL & SERIES - RESISTOR

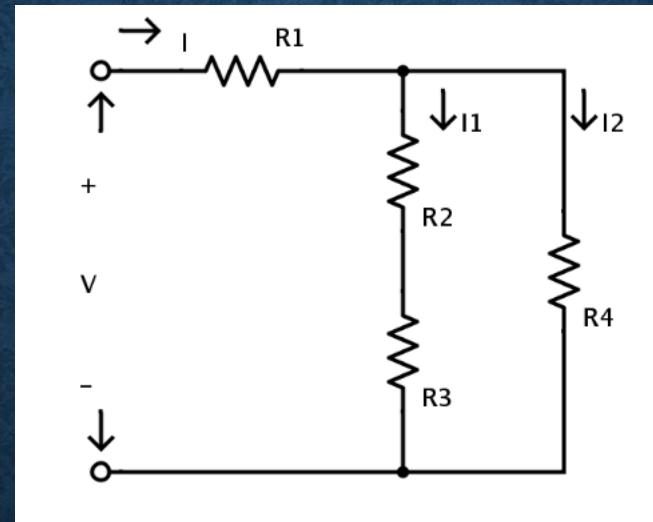


# STEP 1 – SERIES CONDITION

$$R_A = R_2 + R_3$$

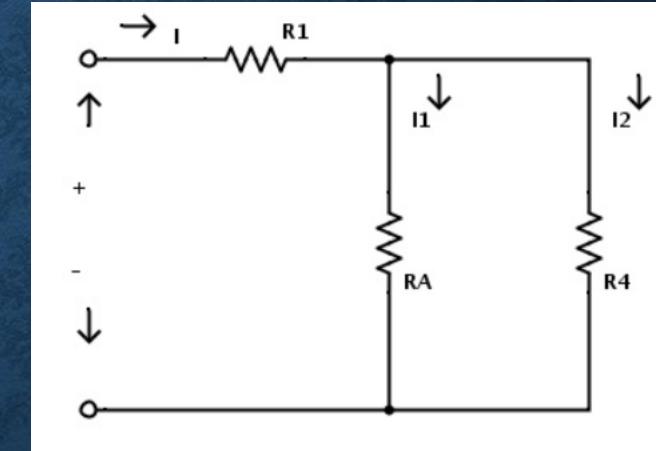


## STEP 2 – PARALLEL CONDITION

$$R_B = R_A \times R_4 / (R_A + R_4)$$

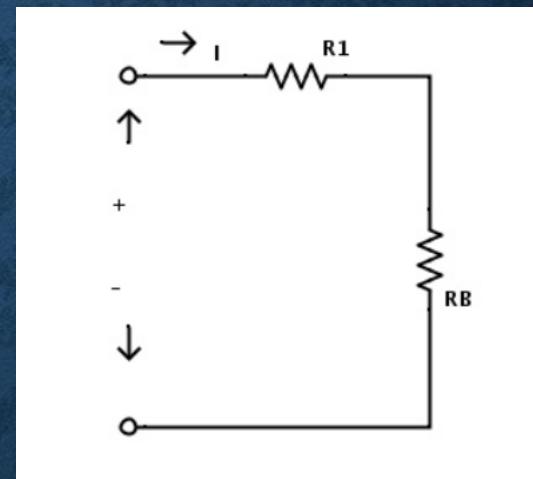


# STEP 3 – SERIES CONDITION

$$R_{EQ} = R_1 + R_B$$

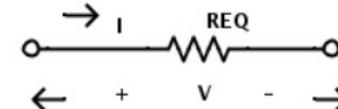


# PARALLEL & SERIAL – RESISTOR #01

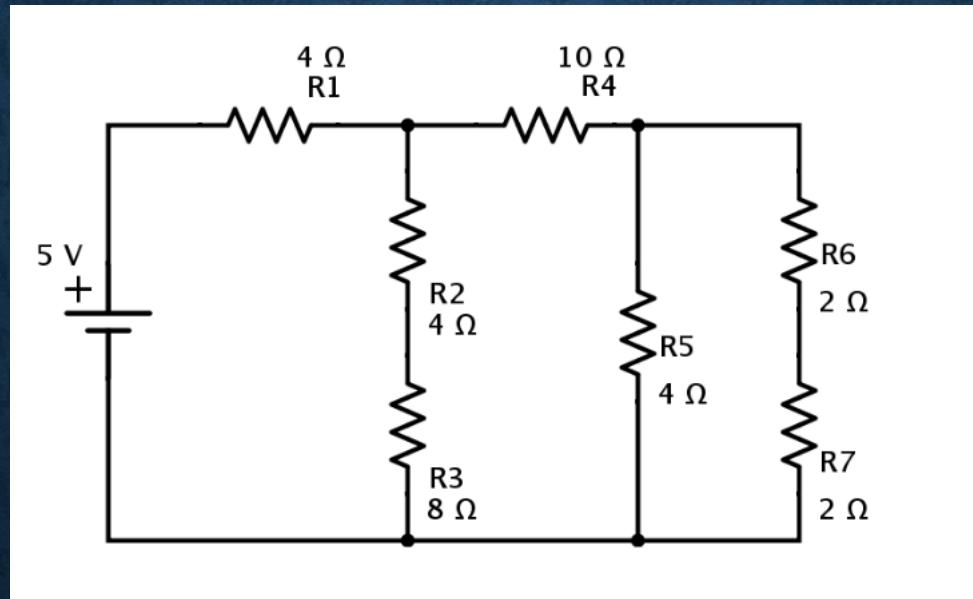

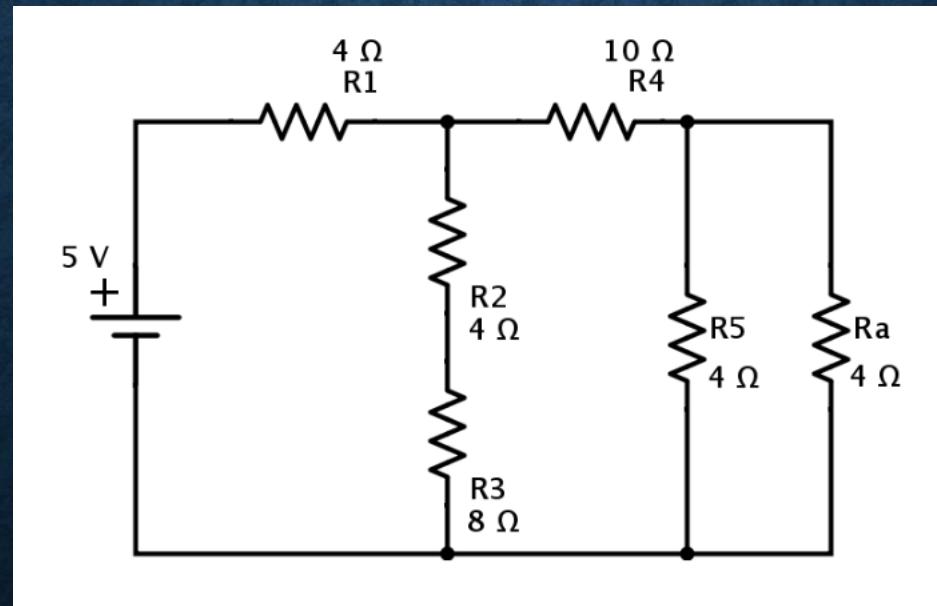
# STEP 1

- Resistors R6 and R7 are in series combination. If the equivalent resistance of R6 and R7 in series is Ra, then,  $R_a = R_6 + R_7 = 2+2 = 4\Omega$



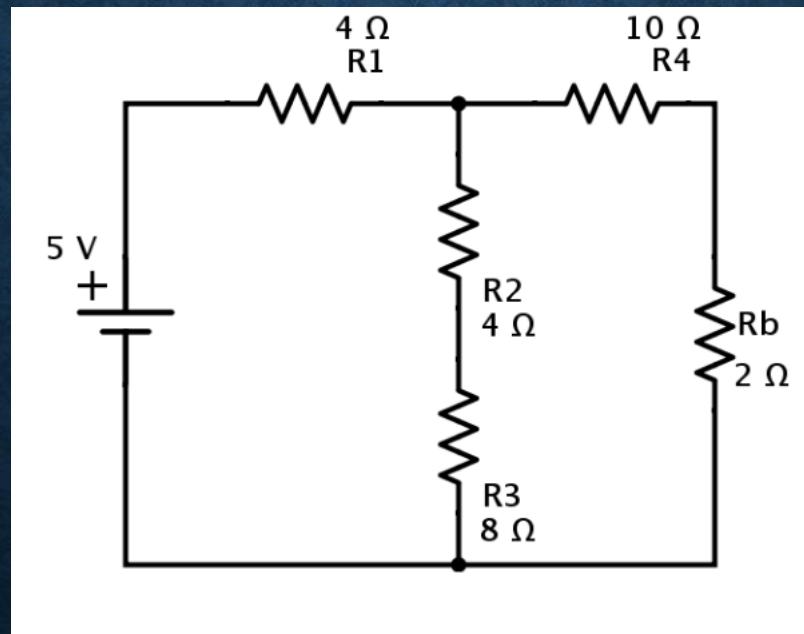
## STEP 2

- Resistors  $R_a$  and  $R_5$  are in parallel combination. Hence the equivalent resistance of  $R_a$  and  $R_5$  is,  $R_b = (R_a \times R_5) / (R_a + R_5) = (4 \times 4) / (4 + 4) = 2\Omega$ .



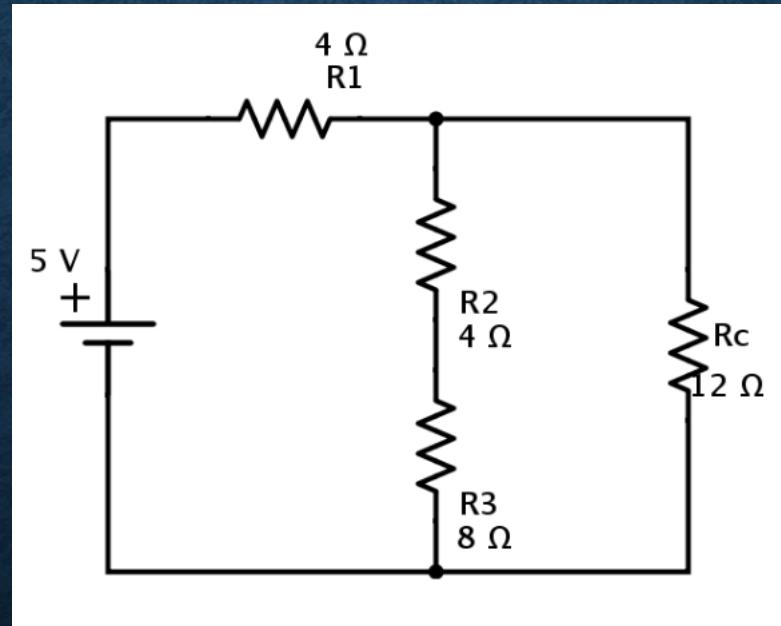
## STEP 3

- Resistors  $R_4$  and  $R_b$  are in series combination,  $R_c = R_4 + R_b = 10 + 2 = 12 \Omega$ .



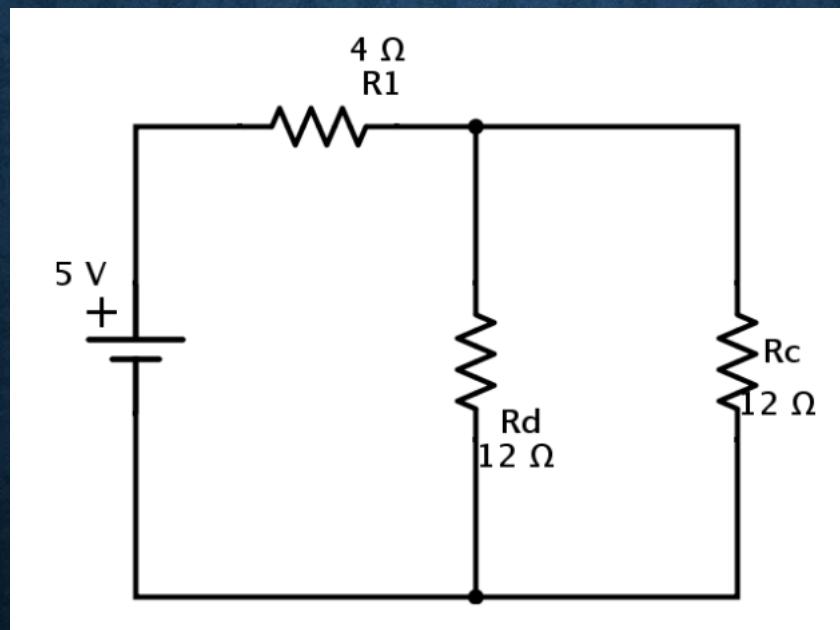
## STEP 4

- Resistors R<sub>2</sub> and R<sub>3</sub> are in series combination. If R<sub>d</sub> is the equivalent resistance of R<sub>2</sub> and R<sub>3</sub> then,  $R_d = R_2 + R_3 = 4 + 8 = 12 \Omega$ .



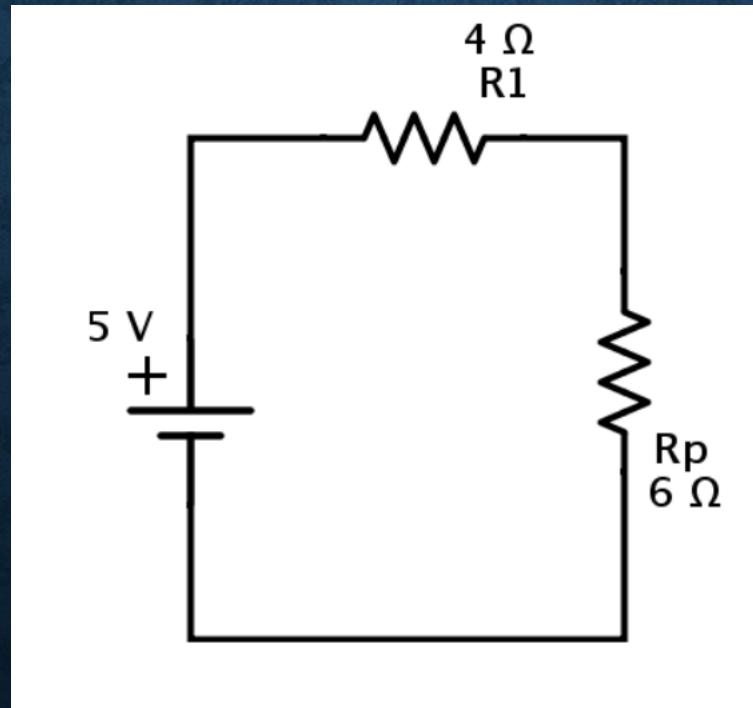
## STEP 5

- Resistors  $R_c$  and  $R_d$  are in parallel combination. Let  $R_p$  be the equivalent resistance of  $R_c$  and  $R_d$  in parallel. Then,  $R_p = (R_c \times R_d) / (R_c + R_d) = (12 \times 12) / (12 + 12) = 6 \Omega$ .



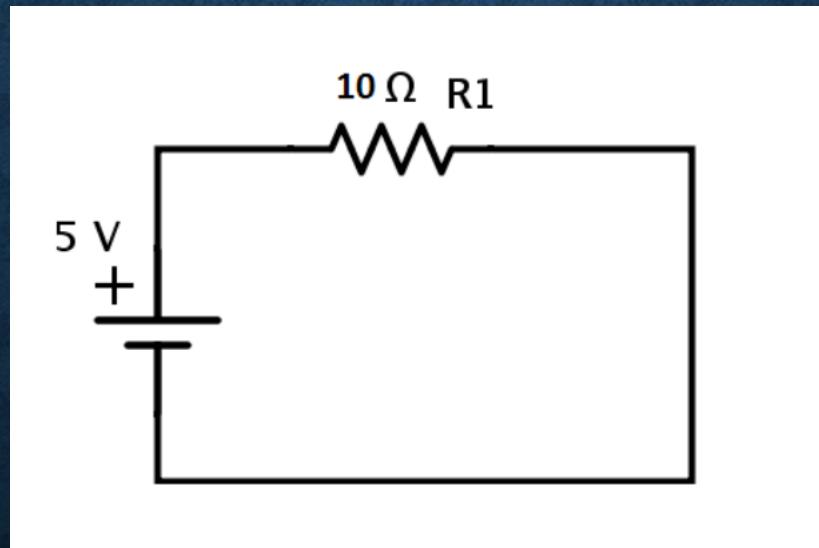
## STEP 6

- Resistors  $R_1$  and  $R_p$  are in series combination. Let  $R_{EQ}$  be the equivalent resistance of this combination. Then,  $R_{EQ} = R_1 + R_p = 4 + 6 = 10 \Omega$ .




- Current in the circuit can be calculated from Ohm's law,  $I = V / R_{EQ} = 5 / 10 = 0.5 \text{ A}$

# PARALLEL & SERIAL – RESISTOR #02

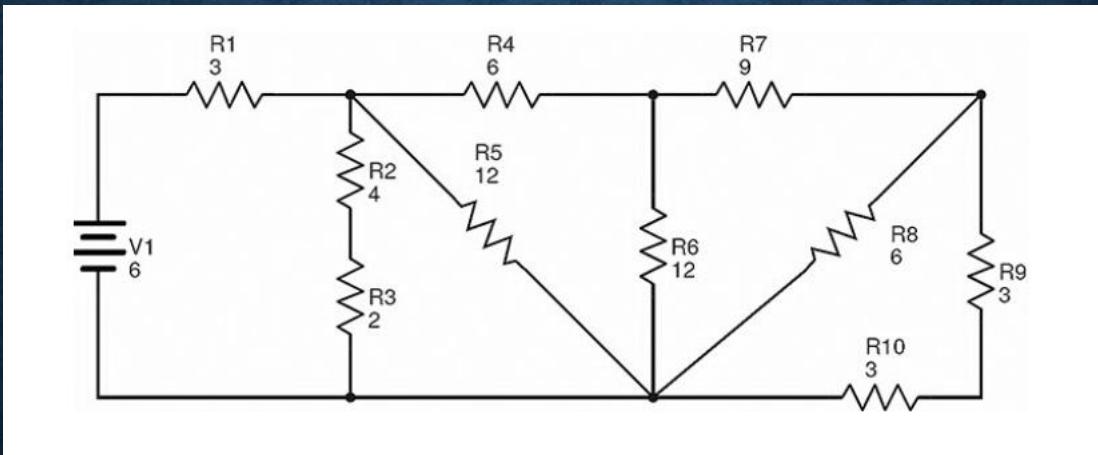

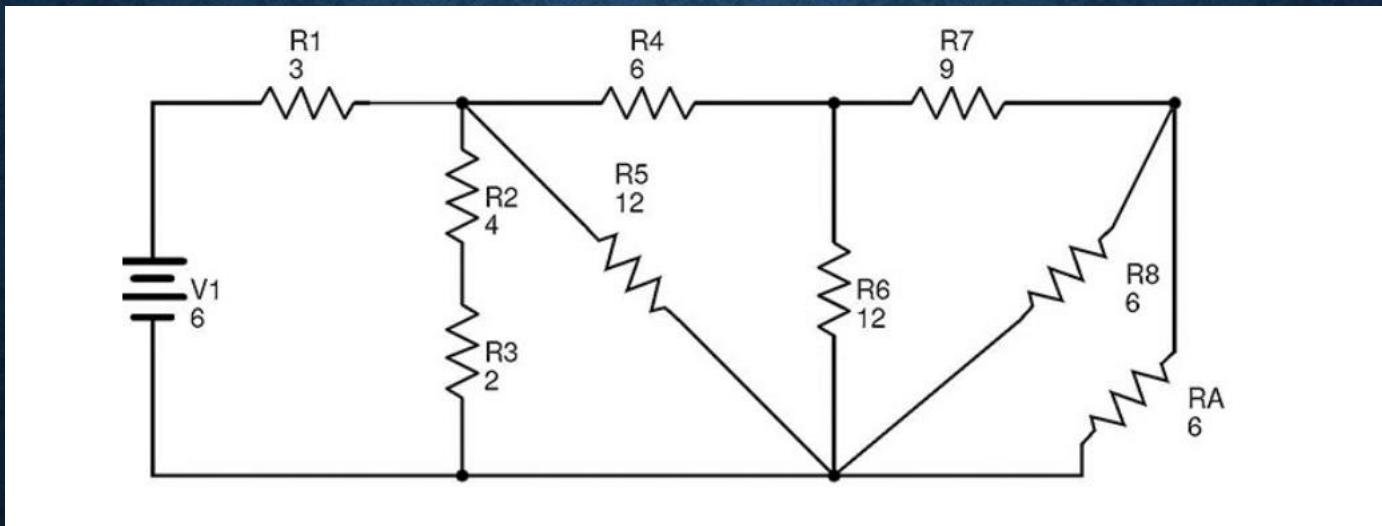
# STEP 1

- Resistors R9 and R10 are in series combination. Let  $R_A$  is the equivalent resistance of this combination, Therefore  $R_A = R9 + R10 = 3 + 3 = 6 \Omega$ .



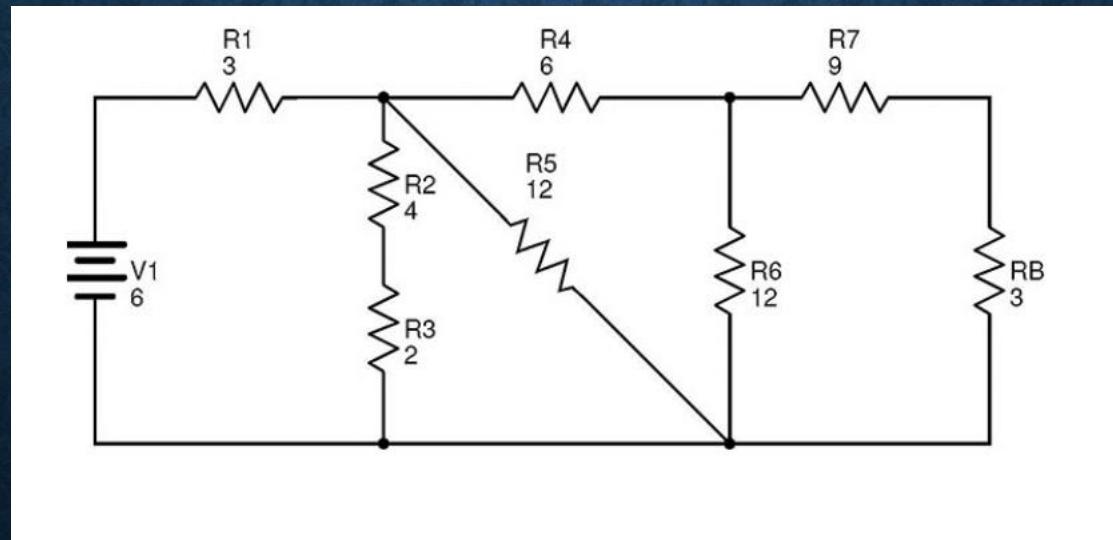
## STEP 2

- Resistors R8 and  $R_A$  are in parallel combination. Then the equivalent resistance of R8 and  $R_A$  is  $R_B = (R8 \times R_A) / (R8 + R_A) = (6 \times 6) / (6 + 6) = 3 \Omega$


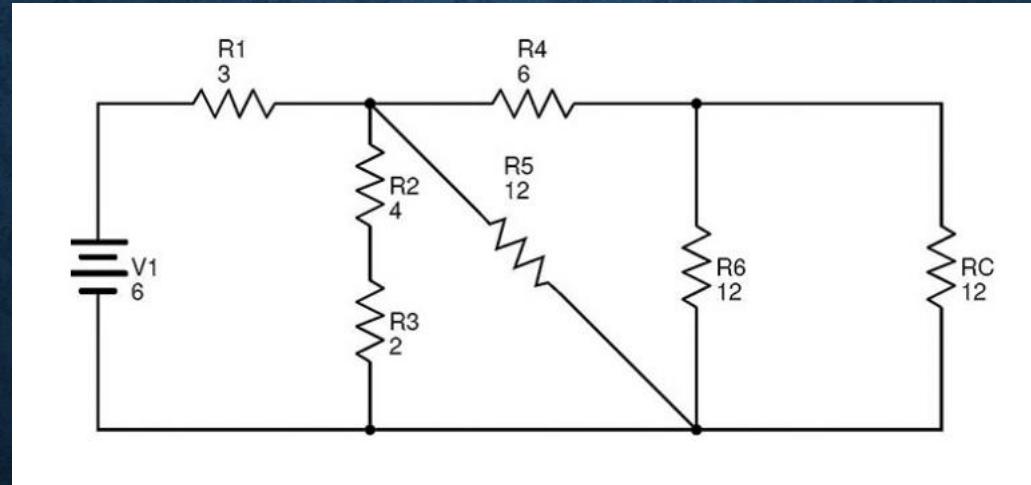
# STEP 3


- Resistors  $R_7$  and  $R_B$  are in series combination,  $R_C = R_7 + R_B = 9 + 3 = 12 \Omega$ .


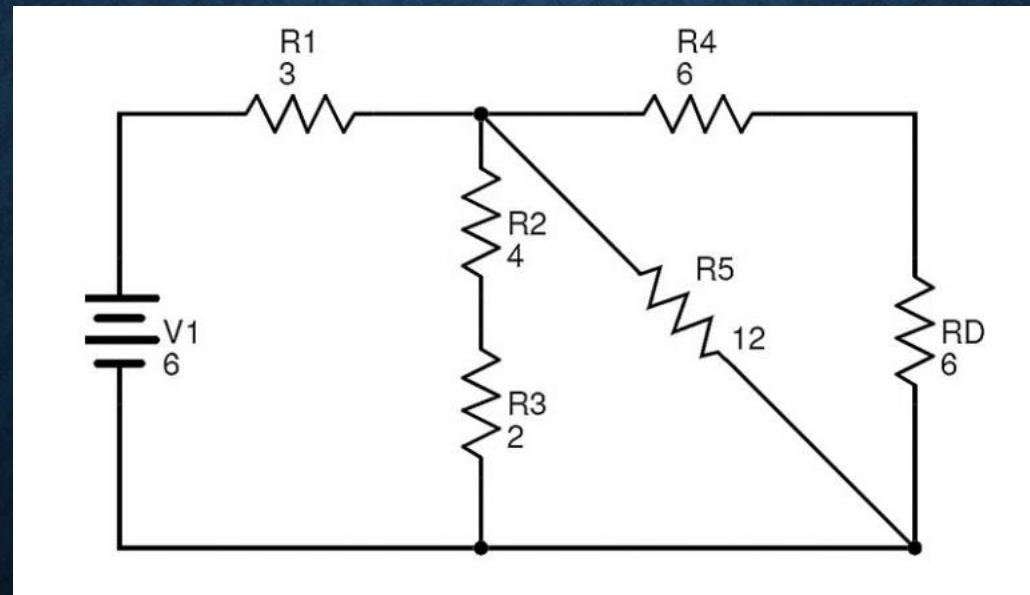
## STEP 4


- It is clear that the resistors  $R_6$  and  $R_c$  are in parallel combination. If  $R_D$  is the equivalent resistance of this combination, then

$$R_D = (R_6 \times R_c) / (R_6 + R_c) = (12 \times 12) / (12 + 12) = 6 \Omega$$


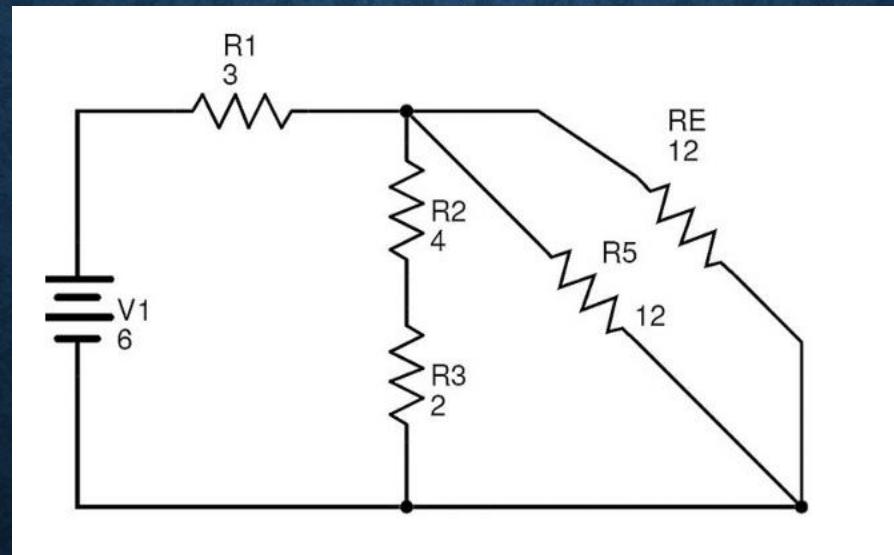
## STEP 5


- Resistors R4 and RD are in series combination. If RE is the equivalent resistance of R4 and RD then,  $R_E = R_4 + R_D = 6 + 6 = 12 \Omega$ .


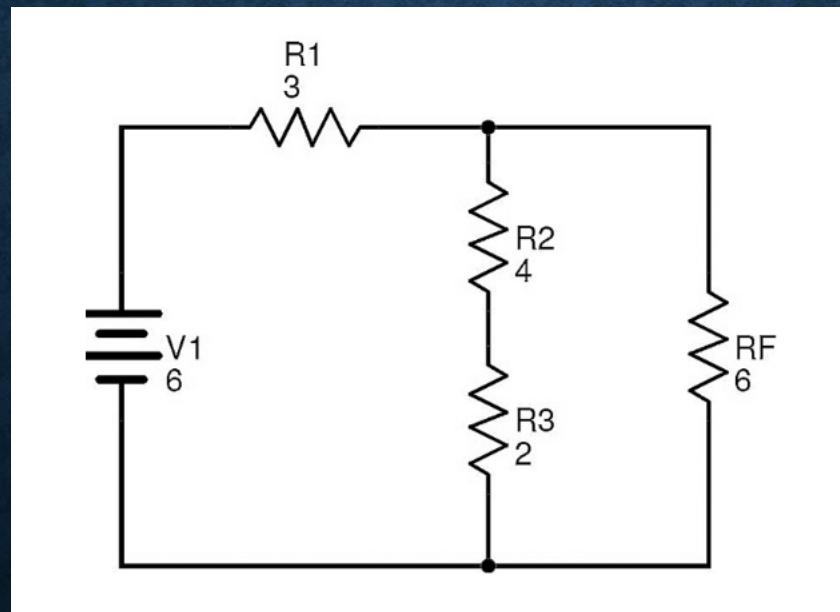
# STEP 6

- Resistors  $R_5$  and  $R_E$  are in parallel combination. Let  $R_F$  be the equivalent resistance of  $R_5$  and  $R_E$  in parallel. Then


$$R_F = (R_5 \times R_E) / (R_5 + R_E) = (12 \times 12) / (12 + 12) = 6 \Omega$$



## STEP 7

- Resistors R<sub>2</sub> and R<sub>3</sub> are in series. If R<sub>G</sub> is the equivalent of this combination, then


$$R_G = R_2 + R_3 = 4 + 2 = 6 \Omega$$

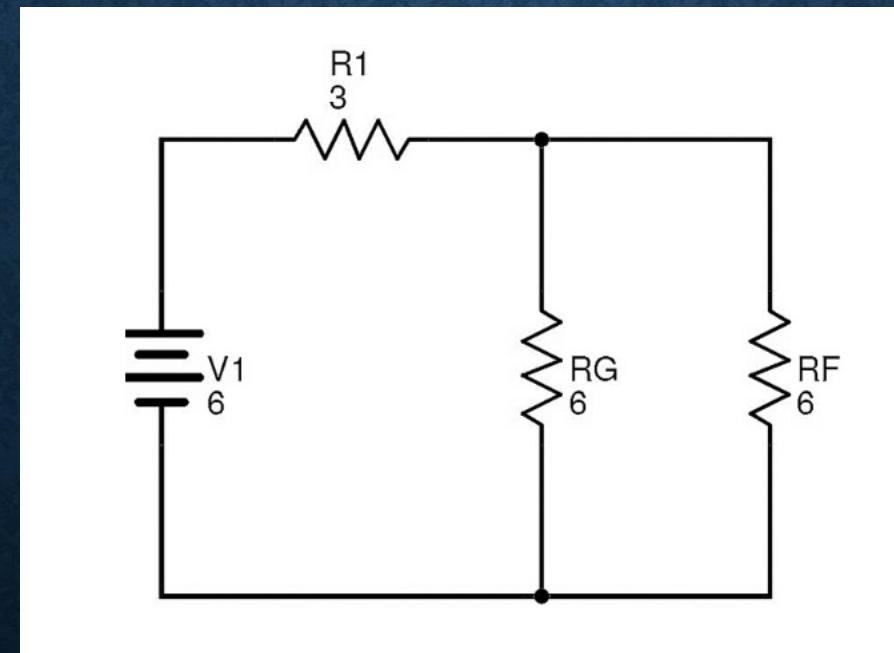
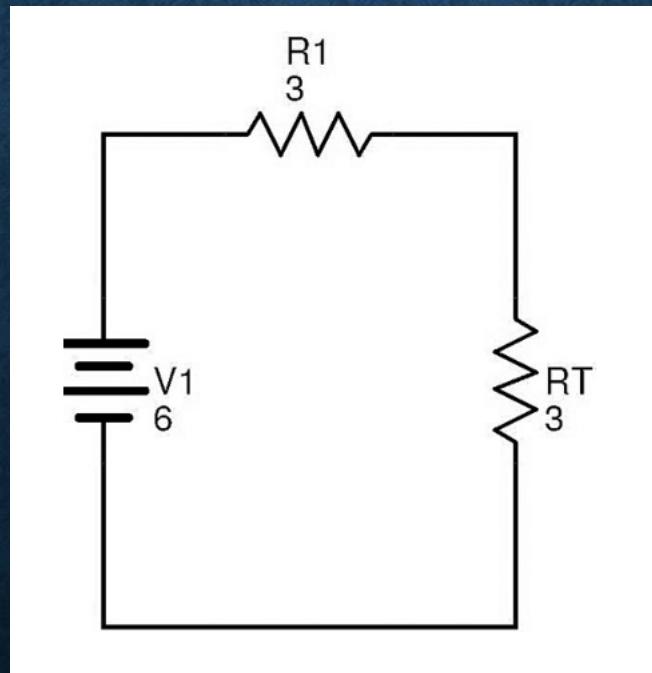
## STEP 8

- Resistors  $R_F$  and  $R_G$  are in parallel. Let  $R_T$  be the equivalent of this combination.

$$R_T = (R_F \times R_G) / (R_F + R_G) = (6 \times 6) / (6 + 6) = 3 \Omega$$



## STEP 9


- Resistors R<sub>1</sub> and R<sub>T</sub> are in series. If R<sub>EQ</sub> is the total circuit equivalent resistance, then

$$R_{EQ} = R_1 + R_T = 3 + 3 = 6 \Omega$$

Finally the above complex circuit can be redrawn as follows

Total current in the circuit can be calculated using Ohm's law

$$I = V_1 / R_{EQ} = 6 / 6 = 1 A$$

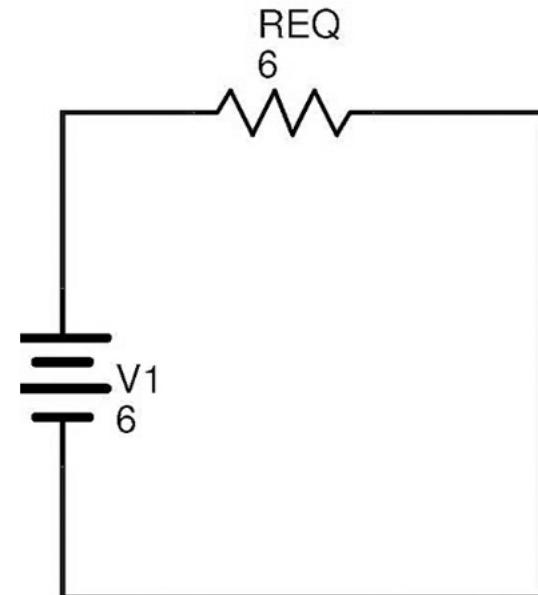

# **SERIES – PARALLEL RESISTOR PROBLEM**

<https://www.youtube.com/watch?v=eFlJy0cPbsY>


# CAPACITOR

- Also known as Condenser
- Used for storage – charge – in the form of electric field


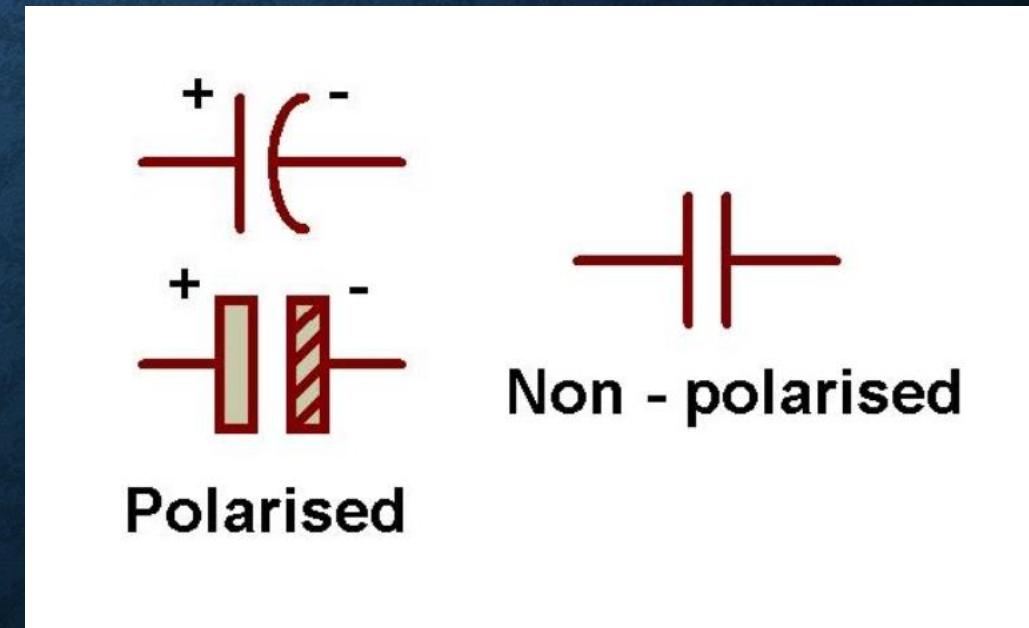
# CAPACITOR


- Capacitor has two parallel metal plates which are not connected to each other.
- The two plates in the capacitor are separated by non conducting medium (insulating medium) this medium is commonly known as **Dielectric**
- Unlike a resistor, an ideal capacitor does not dissipate energy



# TYPES OF CAPACITORS



# PARALLEL CAPACITANCE

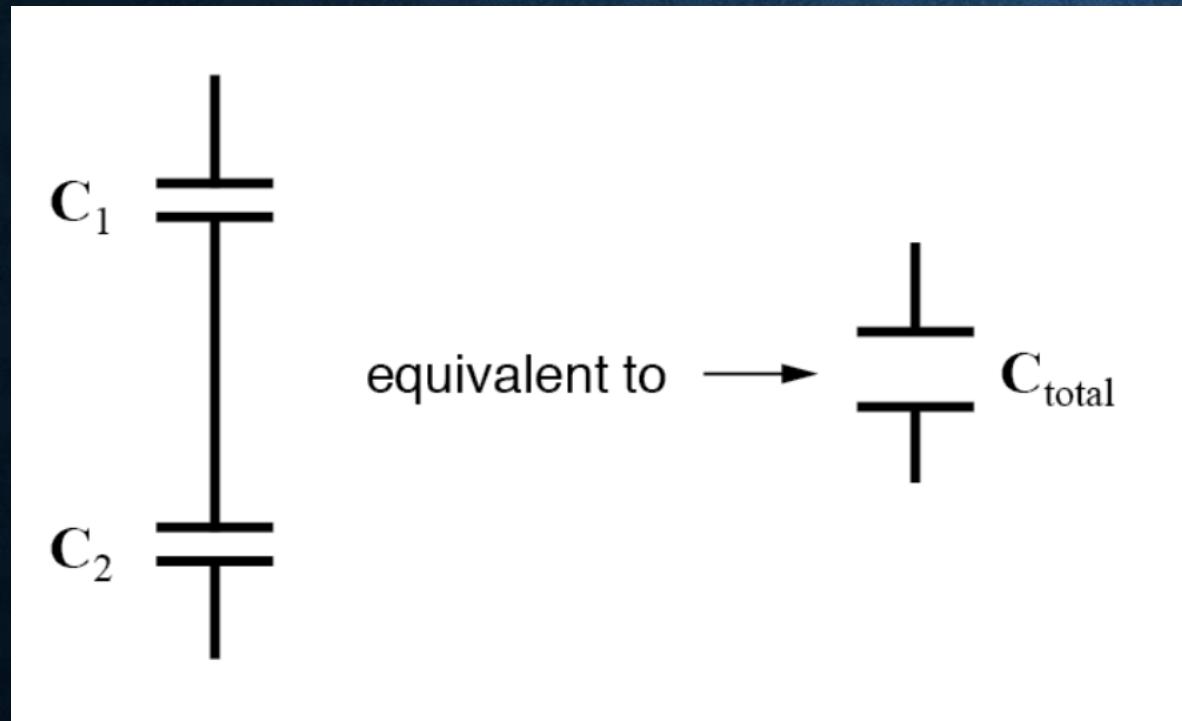


Series Capacitances

$$C_{\text{total}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

Exactly the opposite of the phenomenon exhibited by [resistors](#). With resistors, series connections result in additive values while parallel connections result in diminished values. With capacitors, its the reverse: parallel connections result in additive values while series connections result in diminished values.


# SERIES CAPACITANCE

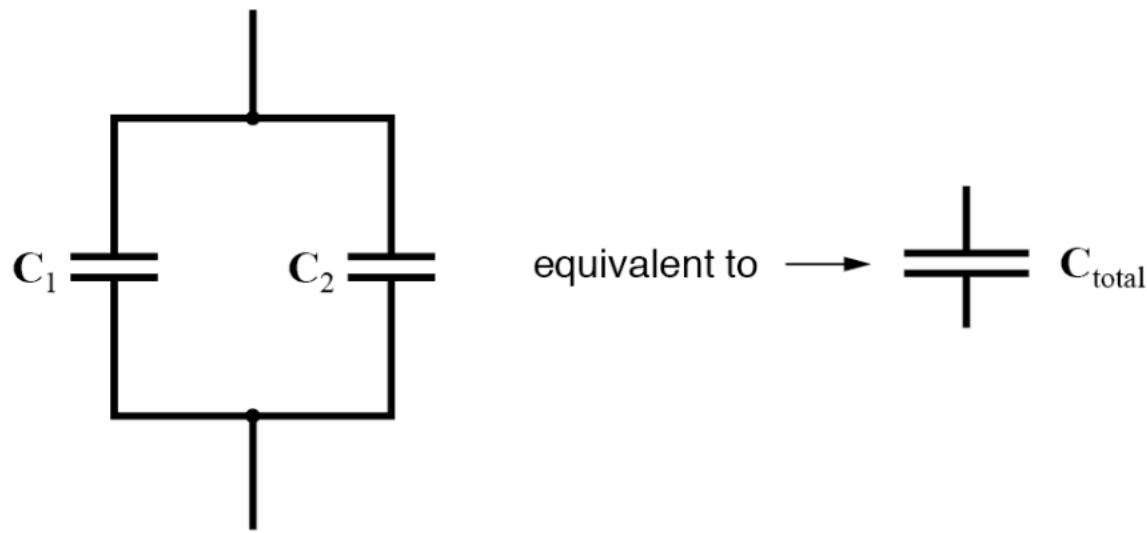


Parallel Capacitances

$$C_{\text{total}} = C_1 + C_2 + \dots + C_n$$

# CAPACITOR IN SERIES

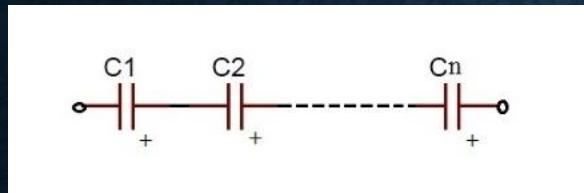
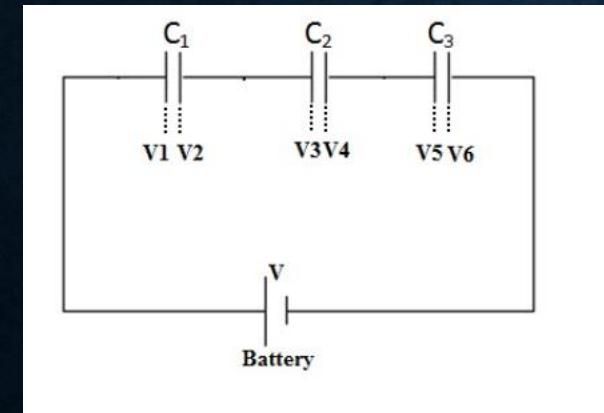
$$Q_T = Q_1 = Q_2 = Q_3 = \dots = Q$$
$$I_C = I_1 = I_2 = I_3 = \dots = I_N$$



Each plate will have different potential. But the magnitude of charge on the plates is same.

**overall potential difference between the plates,  $V_T = V_1 + V_2 + V_3$**

$$Q = CV$$

$$C = Q/V$$

$$C_{eq} = Q/V_1 + Q/V_2 + Q/V_3 \text{ (As charge is same)}$$

$$1/C_{eq} = (V_1 + V_2 + V_3)/Q$$

$$V_T = Q/C_{eq} = Q/C_1 + Q/C_2 + Q/C_3$$

$$\text{Hence, } 1/C_{eq} = 1/C_1 + 1/C_2 + 1/C_3$$

# SERIES CAPACITANCE #01

**Calculate the equivalent capacitance and the individual voltage drops across the set of two capacitors in series have 0.1uF and 0.2uF respectively when connected to a 12V a.c. supply.**

$$1/C_{eq} = 1/C_1 + 1/C_2$$

$$C_{eq} = (C_1 C_2) / (C_1 + C_2)$$

$$C_{eq} = (0.1\text{uF} \cdot 0.2\text{uF}) / (0.1\text{uF} + 0.2\text{uF})$$

$$C_{eq} = 0.066\text{uF} = 66\text{nF}$$

Voltage drops across the two given capacitors in series are,

$$V_1 = (C_2 \cdot V_T) / (C_1 + C_2) = (0.2\text{uF} \cdot 12\text{V}) / (0.1\text{uF} + 0.2\text{uF}) = 8\text{Volts}$$

$$V_2 = (C_1 \cdot V_T) / (C_1 + C_2) = (0.1\text{uF} \cdot 12\text{V}) / (0.1\text{uF} + 0.2\text{uF}) = 4\text{Volts}$$

From these results we observed that the equivalent capacitance 66nF is less than the smallest capacitance 0.1uF of the given two capacitors. The individual voltage drops across the given two capacitors are different

But the sum of individual voltage drops of both the capacitors is equal to the total voltage. i.e  $8\text{V} + 4\text{V} = 12\text{V}$ .

Now we calculate the charge stored in individual capacitor,

$$Q_1 = V_1 \cdot C_1 = 8\text{V} \cdot 0.1\text{uF} = 0.8\text{uC}$$


$$Q_2 = V_2 \cdot C_2 = 4\text{V} \cdot 0.2\text{uF} = 0.8\text{uC}$$

Here we observed that equal charge 0.8uC is stored in both the capacitors C<sub>1</sub> and C<sub>2</sub> which are connected in series.

# PARALLEL CAPACITANCE

- All the capacitors which are connected in parallel have the same voltage and is equal to the VT applied between the input and output terminals of the circuit.
- Then, parallel capacitors have a ‘common voltage’ supply across them .i.e. $VT = V_1 = V_2$  etc.
- The equivalent capacitance,  $C_{eq}$  of the circuit where the capacitors are connected in parallel is equal to the sum of all the individual capacitance of the capacitors added together.
- This is because the top plate of each capacitor in the circuit is connected to the top plate of adjacent capacitors.In the same way the bottom plate of each capacitor in the circuit is connected to the bottom plate of adjacent capacitors

# PARALLEL CAPACITANCE

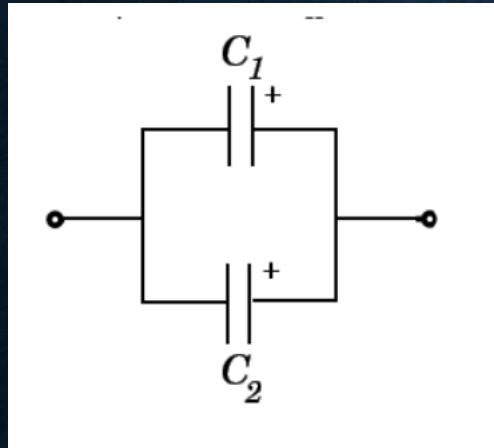

The total charge ( $Q$ ) across the circuit is divided between the two capacitors, means the charge  $Q$  distributes itself between the capacitors connected in parallel. charge  $Q$  is equal to the sum of all the individual capacitor charges.

Thus  $Q=Q_1+Q_2$

$$Q=C_{eq} VT$$

$$\text{Here, } Q = Q_1 + Q_2$$

$$C_{eq} VT = C_1 \times V_1 + C_2 \times V_2$$

$$\text{Since } VT = V_1 = V_2 = V$$

$$C_{eq} VT = C_1 \times V + C_2 \times V$$

$$C_{eq} VT = (C_1 + C_2)V$$

$$\text{Hence } C_{eq} = C_1 + C_2$$

**Consider the capacitance values of the two capacitors  $C_1 = 0.2\text{uF}$  and  $C_2 = 0.3\text{uF}$  which are shown in above figure 4. Now calculate the equivalent capacitance of the circuit**

$$C_{eq} = C_1 + C_2$$


$$C_{eq} = 0.2\text{uF} + 0.3\text{uF}$$

$$C_{eq} = 0.5\text{uF}$$

# **VIDEOS -RELATED - CAPACITOR**

- Capacitor – in detail <https://www.youtube.com/watch?v=BimpNou0orc>
- Capacitor in Series & Parallel - <https://www.youtube.com/watch?v=zaT4JorVUz0>
- Capacitor in Series & Parallel - <https://www.youtube.com/watch?v=a-gPuw6JsxQ>

# INDUCTOR & ITS TYPES

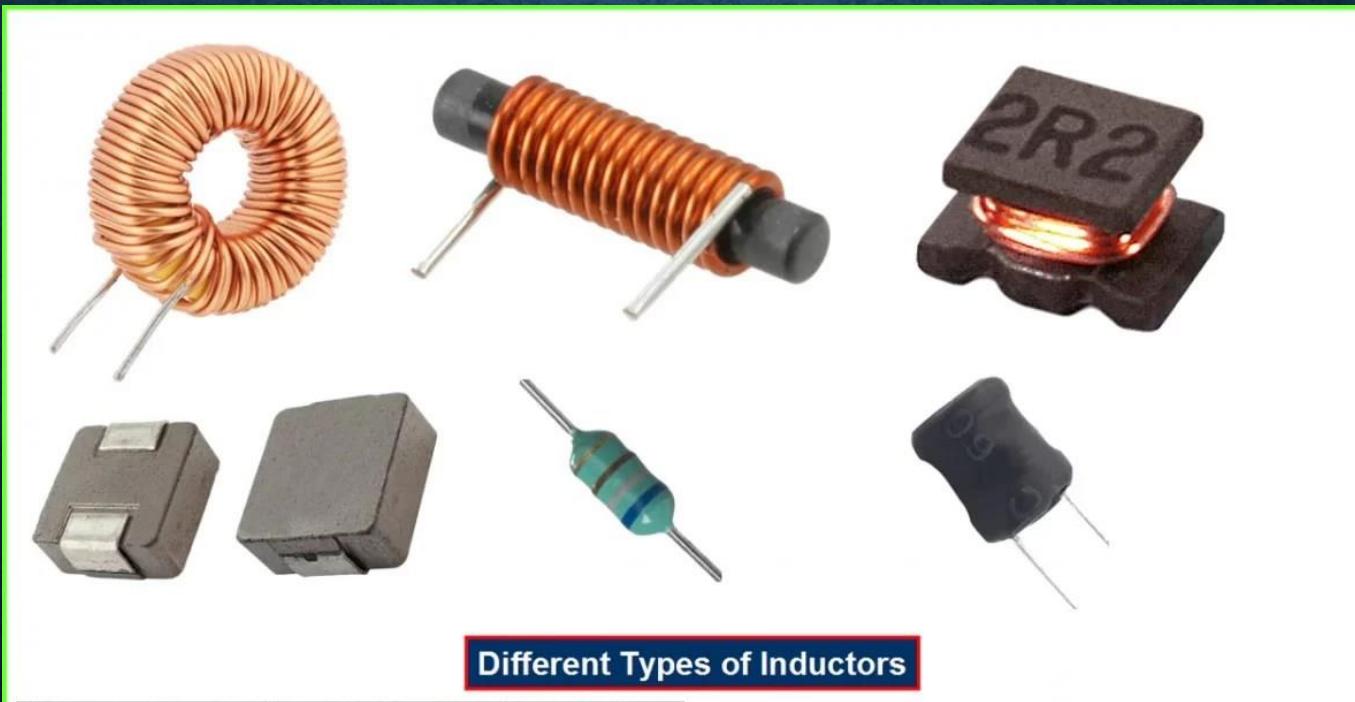


Different Types of Inductors


# INDUCTOR

- An inductor, also called a coil, choke, or reactor, is a passive two-terminal electrical component that stores energy in a magnetic field when electric current flows through it.
- An inductor typically consists of an insulated wire wound into a coil.
- An inductor is characterized by its inductance: ratio of the voltage to the rate of change of current.
- Unit of inductance is the henry (H)
- In the measurement of magnetic circuits, it is equivalent to weber/ampere.
- Inductors have values that typically range from  $1 \mu\text{H}$  ( $10^{-6} \text{ H}$ ) to 20 H.
- Many inductors have a magnetic core made of iron or ferrite inside the coil, which serves to increase the magnetic field and thus the inductance.
- **Inductance** – property that exhibits opposition to the change of current, measured in **henrys (H)**.

# INDUCTOR EQUATION

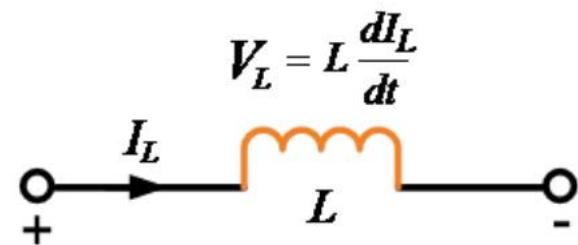


Voltage Across an Inductor

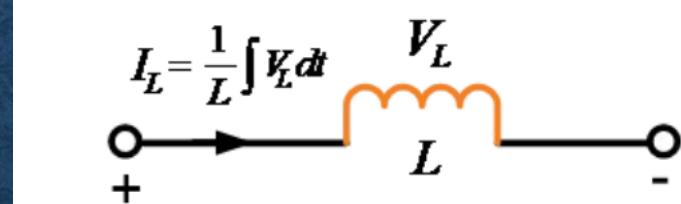

Current Through an Inductor

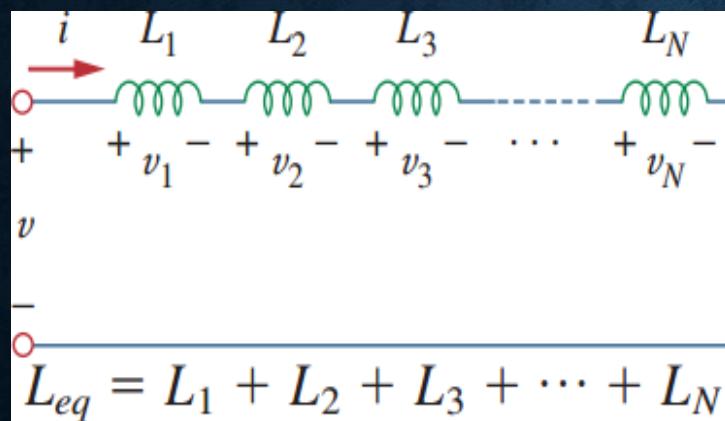
# SERIES & PARALLEL - INDUCTOR

Inductors in **series**, add. In **parallel**, they act like resistors in **parallel**.



$$v = L \frac{di}{dt}$$
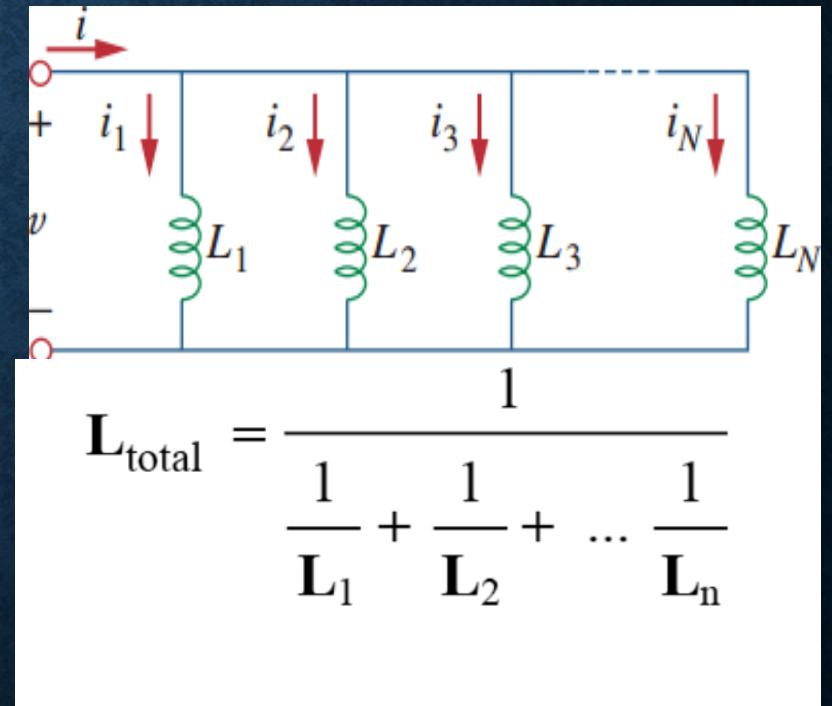
$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$



# INDUCTOR SERIES

- Three inductors of 10mH, 40mH and 50mH are connected together in a series combination with no mutual inductance between them. Calculate the total inductance of the series combination.

$$L_T = L_1 + L_2 + L_3 = 10\text{mH} + 40\text{mH} + 50\text{mH} = 100\text{mH}$$

- Two inductors of 10mH respectively are connected together in a series combination so that their magnetic fields aid each other giving cumulative coupling. Their mutual inductance is given as 5mH. Calculate the total inductance of the series combination.

$$L_T = L_1 + L_2 + 2M$$

$$L_T = 10\text{mH} + 10\text{mH} + 2(5\text{mH})$$

$$L_T = 30\text{mH}$$

# INDUCTOR SERIES

- Two coils connected in series have a self-inductance of 20mH and 60mH respectively. The total inductance of the combination was found to be 100mH. Determine the amount of mutual inductance that exists between the two coils assuming that they are aiding each other.

$$L_T = L_1 + L_2 \pm 2M$$

$$100 = 20 + 60 + 2M$$

$$2M = 100 - 20 - 60$$

$$\therefore M = \frac{20}{2} = 10\text{mH}$$

# INDUCTOR PARALLEL #01

- Three inductors of 60mH, 120mH and 75mH respectively, are connected together in a parallel combination with no mutual inductance between them. Calculate the total inductance of the parallel combination in millihenries.

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\therefore L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}} = \frac{1}{\frac{1}{60\text{mH}} + \frac{1}{120\text{mH}} + \frac{1}{75\text{mH}}}$$

$$L_T = \frac{1}{38.333} = 26\text{mH}$$

# INDUCTOR PARALLEL #02

- Two inductors whose self-inductances are of 75mH and 55mH respectively are connected together in parallel aiding. Their mutual inductance is given as 22.5mH. Calculate the total inductance.

$$L_T = \frac{L_1 \times L_2 - M^2}{L_1 + L_2 - 2M}$$

$$L_T = \frac{75\text{mH} \times 55\text{mH} - 22.5\text{mH}^2}{75\text{mH} + 55\text{mH} - 2 \times 22.5\text{mH}}$$

$$L_T = 42.6\text{mH}$$

# INDUCTOR – SERIES & PARALLEL #01


- Two inductors whose self-inductances are of 75mH and 55mH respectively are connected together in parallel aiding. Their mutual inductance is given as 22.5mH. Calculate the total inductance.

$$L_T = \frac{L_1 \times L_2 - M^2}{L_1 + L_2 - 2M}$$

$$L_T = \frac{75\text{mH} \times 55\text{mH} - 22.5\text{mH}^2}{75\text{mH} + 55\text{mH} - 2 \times 22.5\text{mH}}$$

$$L_T = 42.6\text{mH}$$

# INDUCTOR – SERIES & PARALLEL #02

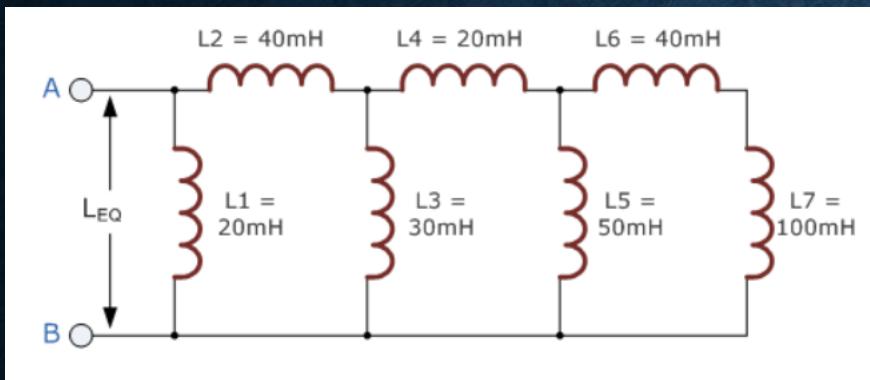

Calculate the first inductor branch L<sub>A</sub>, (Inductor L<sub>5</sub> parallel with inductors L<sub>6</sub> and L<sub>7</sub>)

$$L_A = \frac{L_5 \times (L_6 + L_7)}{L_5 + L_6 + L_7} = \frac{50\text{mH} \times (40\text{mH} + 100\text{mH})}{50\text{mH} + 40\text{mH} + 100\text{mH}} = 36.8\text{mH}$$

Calculate the second inductor branch L<sub>B</sub>, (Inductor L<sub>3</sub> in parallel with inductors L<sub>4</sub> and L<sub>A</sub>)

$$L_B = \frac{L_3 \times (L_4 + L_A)}{L_3 + L_4 + L_A} = \frac{30\text{mH} \times (20\text{mH} + 36.8\text{mH})}{30\text{mH} + 20\text{mH} + 36.8\text{mH}} = 19.6\text{mH}$$

$$L_{EQ} = \frac{L_1 \times (L_2 + L_B)}{L_1 + L_2 + L_B} = \frac{20\text{mH} \times (40\text{mH} + 19.6\text{mH})}{20\text{mH} + 40\text{mH} + 19.6\text{mH}} = 15\text{mH}$$

# VIDEOS - INDUCTOR

- Inductor & its working - <https://www.youtube.com/watch?v=KSylo0ln5FY>
- Series & Parallel inductor - <https://www.youtube.com/watch?v=jgKoRUBX0Y4>

# RESISTOR VS CAPACITOR VS INDUCTOR

<b>Relation</b>	<b>Resistor (<math>R</math>)</b>	<b>Capacitor (<math>C</math>)</b>	<b>Inductor (<math>L</math>)</b>
$v-i$ :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$ :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
$p$ or $w$ :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} Cv^2$	$w = \frac{1}{2} Li^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit

## Capacitors

Energy stored in:

---

Electric field

When connected  
to voltage:

---

V increases  
I decreases

Time constant for  
charging/discharging:

---

RC

When disconnected  
from power:

Maintains voltage

## Inductors

Magnetic field

I increases  
V decreases

RL

Maintains current

# **OTHER ELECTRONIC COMPONENTS**

- Decade Resistance Box
- Decade Capacitance Box
- Decade Inductance Box
- Regulated Power Supply
- Function Generator
- Multimeter
- Cathode Ray Oscilloscope

# DECADE BOX



# REGULATED POWER SUPPLY


- A **regulated power supply** converts unregulated AC (Alternating Current) to a constant DC (Direct Current).
- A regulated power supply is used to ensure that the output remains constant even if the input changes
- Basic building blocks of a regulated DC power supply

A step-down transformer

A rectifier

A DC filter

A regulator

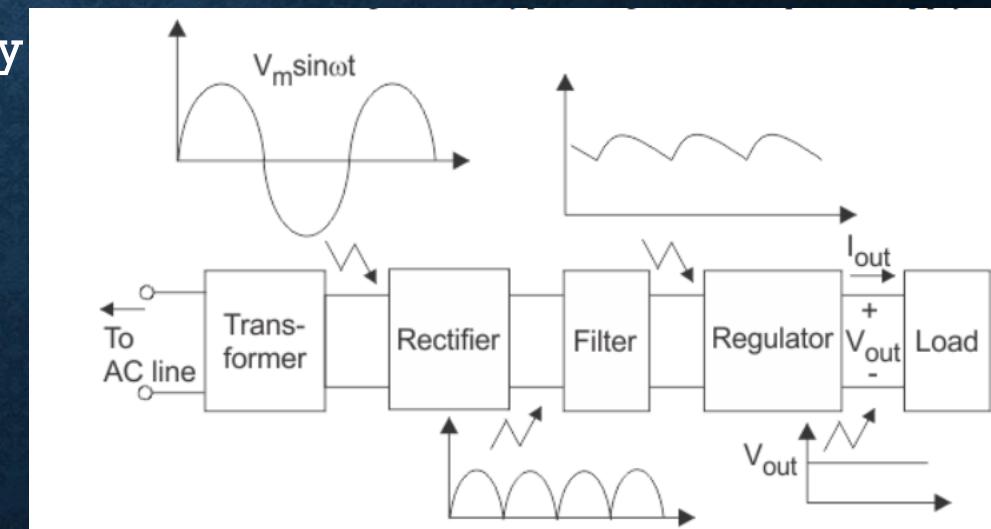

Components of typical linear power supply

# FUNCTION GENERATOR

- Generates a variety of signals for testing and troubleshooting electronic circuits
- The most common types of signals are Triangular Wave, Sine Wave, Square Wave and Sawtooth Wave.



# MULTI-METER

A multimeter is a combination of Voltmeter, Ammeter and Ohmmeter

Multimeters can measure values in both AC and DC



Analog Multimeter



Digital Multimeter



Bench Multimeter

# OSCILLOSCOPE

- Observing continuously varying signals is an Oscilloscope
- We can observe the changes in an electrical signal like voltage, over time.
- Oscilloscopes are used in a wide range of field like Medical, Electronic, Automobile, Industrial and Telecommunication Applications.
- Oscilloscopes are made up of Cathode Ray Tube (CRT) displays but nowadays, almost all Oscilloscopes are Digital Oscilloscopes with advanced features like storage and memory



# CATHODE RAY OSCILLOSCOPE

- CRO stands for a cathode ray oscilloscope
- It is typically divided into four sections which are display, vertical controllers, horizontal controllers, and Triggers
- Most of the oscilloscopes are used the probes and they are used for the input of any instrument.
- We can analyze the waveform by plotting amplitude along with the x-axis and y-axis.
- The applications of CRO are mainly involved in the radio, TV receivers, also in laboratory work involving research and design

# CATHODE RAY OSCILLOSCOPE

- The oscilloscope observes the changes in the electrical signals over time, thus the voltage and time describe a shape and it is continuously graphed beside a scale.
- By seeing the waveform, we can analyze some properties like amplitude, frequency, rise time, distortion, time interval, and etc.
- How to use Function Generator & CRO?  
<https://www.youtube.com/watch?v=yQiYDGVUHgA>

# ELECTRO-MECHANICAL COMPONENTS

- An electromechanical component is one that uses an electrical signal to cause some kind of mechanical change, such as motor turning.
- These normally use an electrical current to create a magnetic field which causes a physical movement.
- All types of relays and switches are available in this category

# SWITCHES - EM

- An electromechanical switch is a manually operated switch used to make or break the connection in an electric circuit by means of magnetic field and moving contacts.



# RELAYS - EM

- Relays are designed to emulate higher-level switch functions.
- Relays are normally multipole, double throw devices and are usually designed for low-current switching.
- Relays are used extensively for control applications and are found in nearly every electromechanical appliance manufactured.
- How relay works?

<https://www.youtube.com/watch?v=Ca20ktPygY8>



**Types of Relays**

